

# The effect of AM noise on correlation PM noise measurements

## 1/f noise in RF and microwave amplifiers

Enrico Rubiola, Rodolphe Boudot, Yannick Gruson

FEMTO-ST Institute, Besançon, France  
CNRS and Université de Franche Comté


TimeNav'07 – May 31, 2007

### Outline

- \* Part 1 – The effect of AM noise ...
- \* Part 2 – Amplifier noise ...

# 1 - The effect of AM noise on correlation phase noise measurements
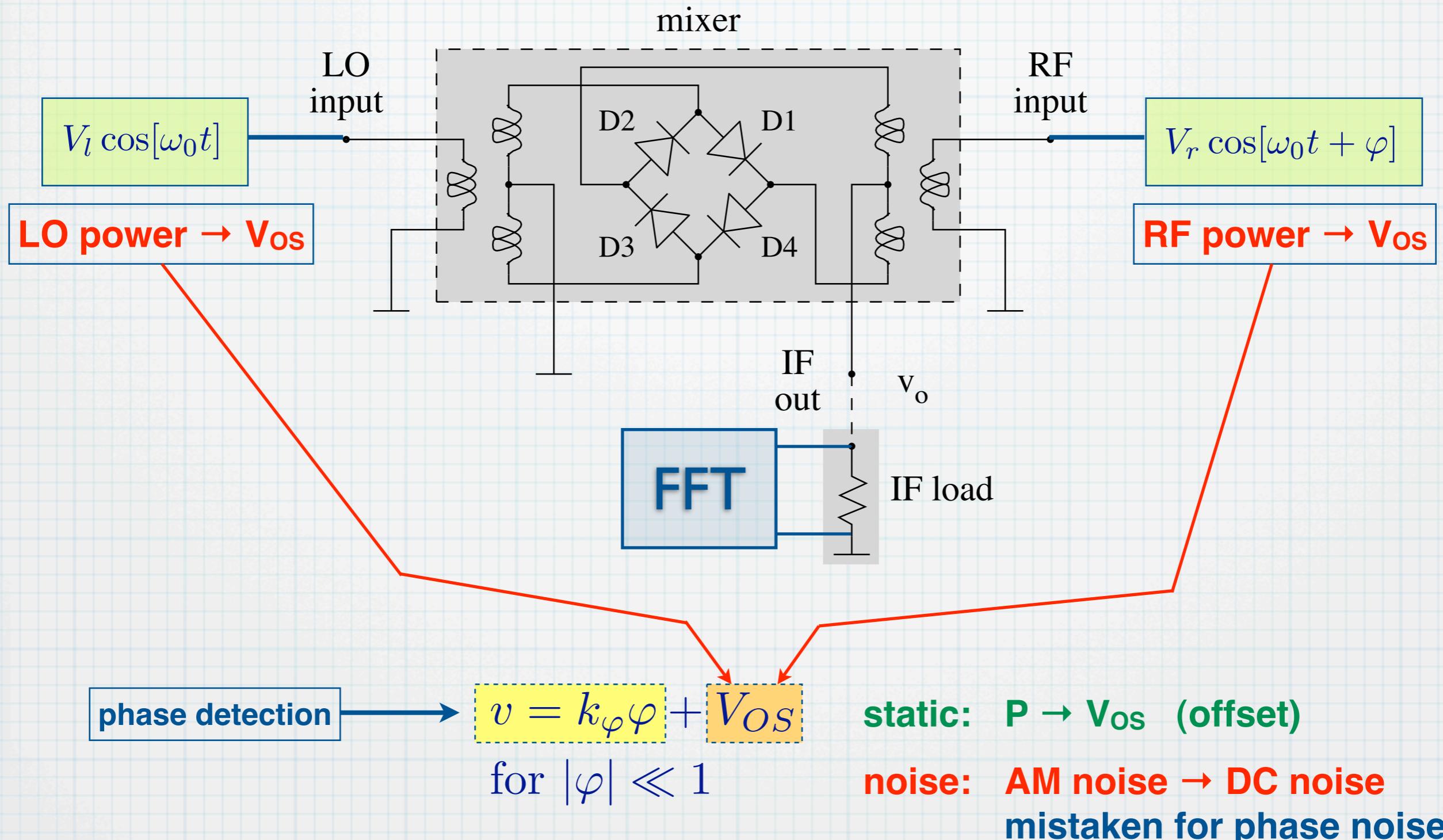
# Effect of AM noise on a saturated mixer




**origin:** diode and balun asymmetry

**RF mixer:** balun asymmetry ≈ const. vs. frequency

**microwave:** balun asymmetry depends on frequency
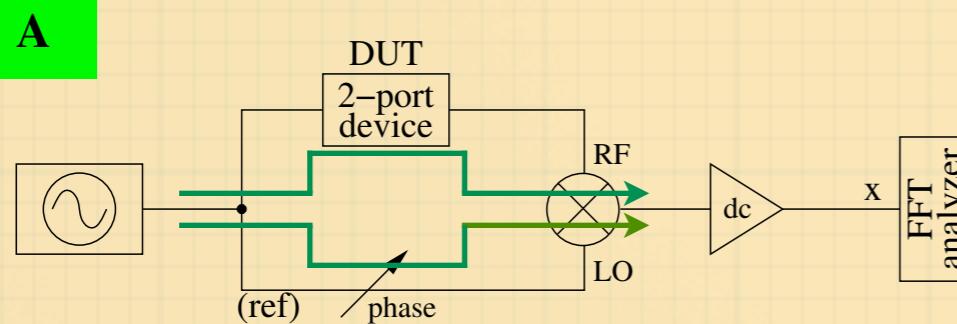
# The AM noise propagates through the system


A null of AM sensitivity (sweet point) can be found in some mixers




tip: use a phase offset, or a DC bias at the mixer IF

$$v_o(t) = k_\varphi \varphi(t) + k_{lr} \alpha_l(t)$$

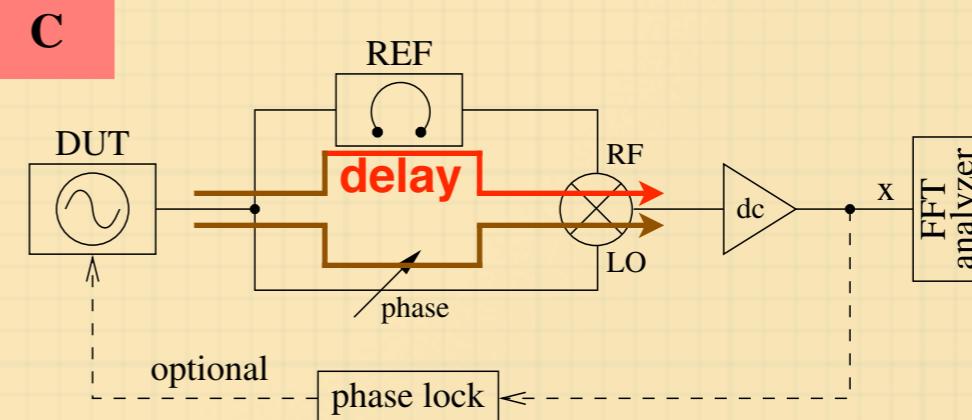A delay de-correlates the two inputs, thus it destroys the sweet point



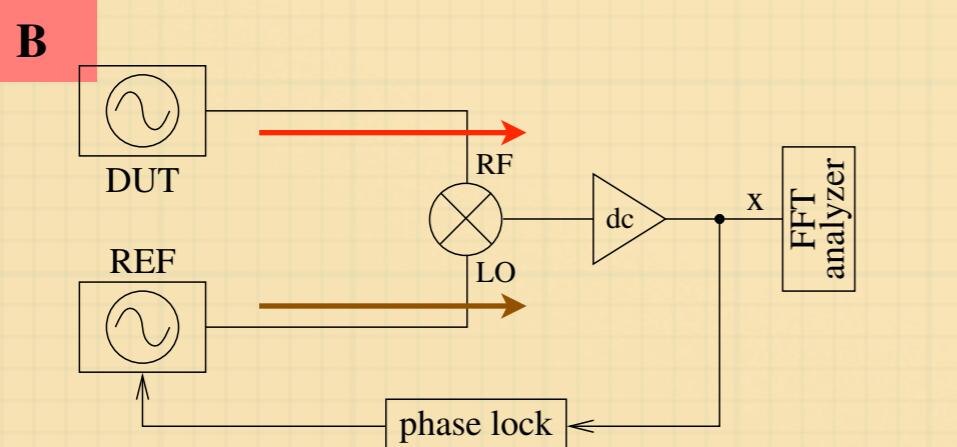
$$v_o(t) = k_\varphi \varphi(t) + k_l \alpha_l(t) + k_r \alpha_r(t)$$



$$v_o(t) = k_\varphi \varphi(t) + k_l \alpha_l(t) + k_r \alpha_r(t)$$

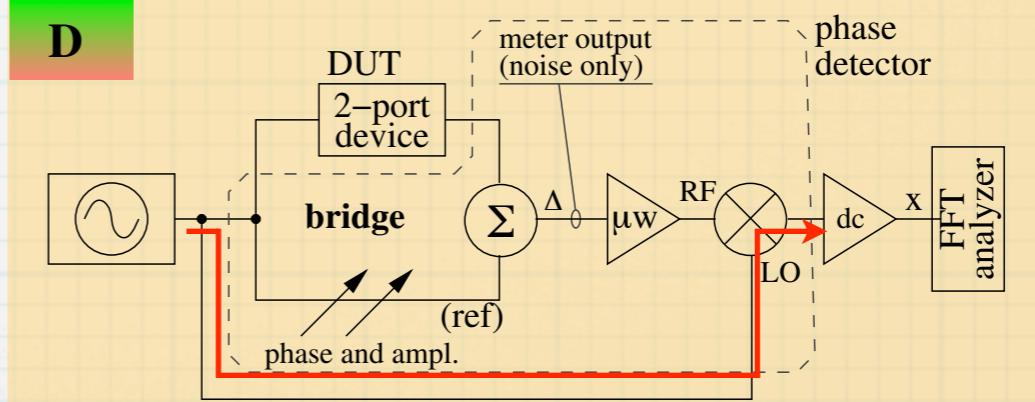
With two separated inputs, the effect of AM noise adds up



$$v_o(t) = k_\varphi \varphi(t) + k_{sd} \alpha(t)$$

In a bridge, the AM noise propagates to the output only through the LO. The effect is strongly reduced by the RF amplification before detecting
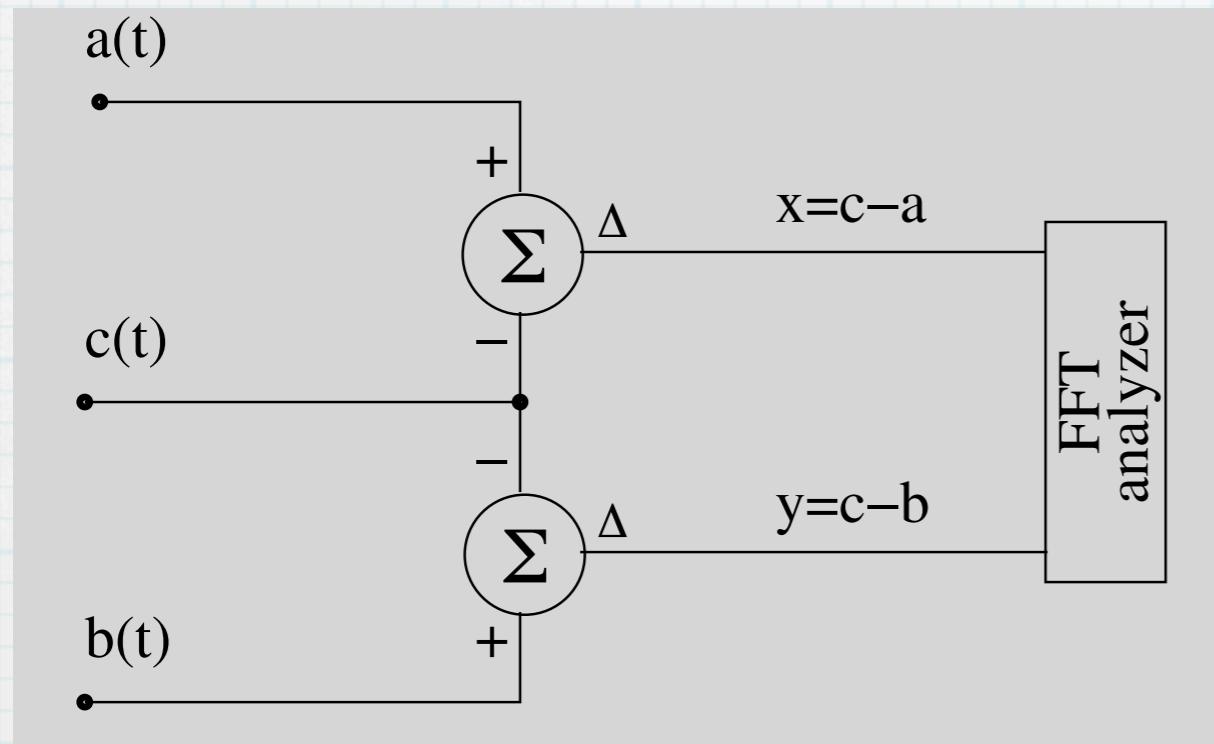
# Basics of correlation spectrum measurements



## phase noise measurements

DUT noise, normal use	$a, b$ $c$	instrument noise DUT noise
background, ideal case	$a, b$ $c = 0$	instrument noise no DUT
background, with AM noise	$a, b$ $c \neq 0$	instrument noise AM-to-DC noise

$$S_{yx} = \mathbb{E} \{ Y X^* \}$$

$$S_{yx} = \langle Y X^* \rangle_m$$

W. K. theorem

measured,  $m$  samples

$a, b$  and  $c$  are uncorrelated

expand  $X = C - A$  and  $Y = C - B$

$$S_{yx} = S_{cc}$$

$$S_{yx} = S_{cc} + O(\sqrt{1/m})$$


$a, b, c$  independent

measured,  $m$  samples



Averaging on a sufficiently large number  $m$  of spectra is necessary to reject the single-channel noise
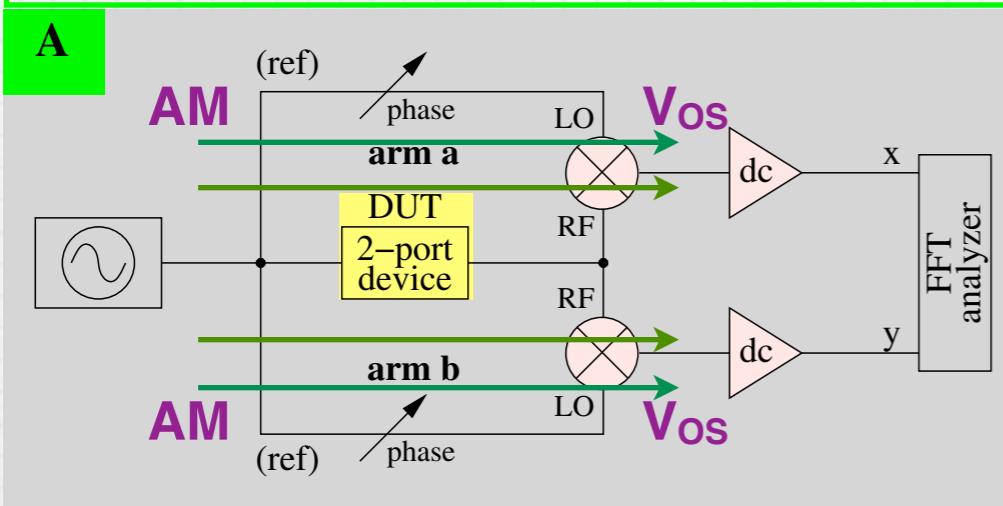
# The AM noise in a correlation system


Should set both channels at the sweet point, if exists



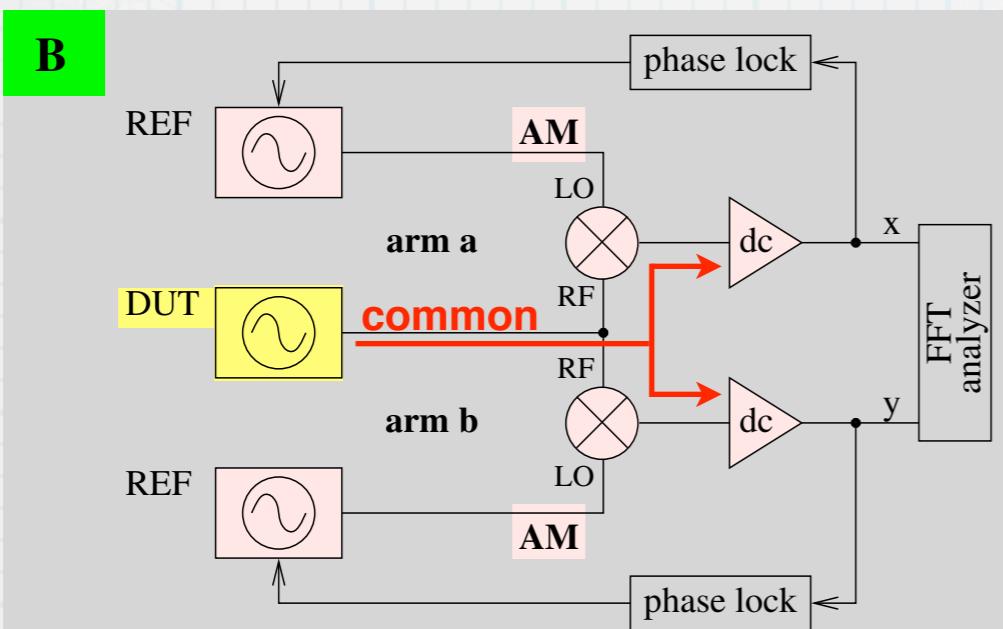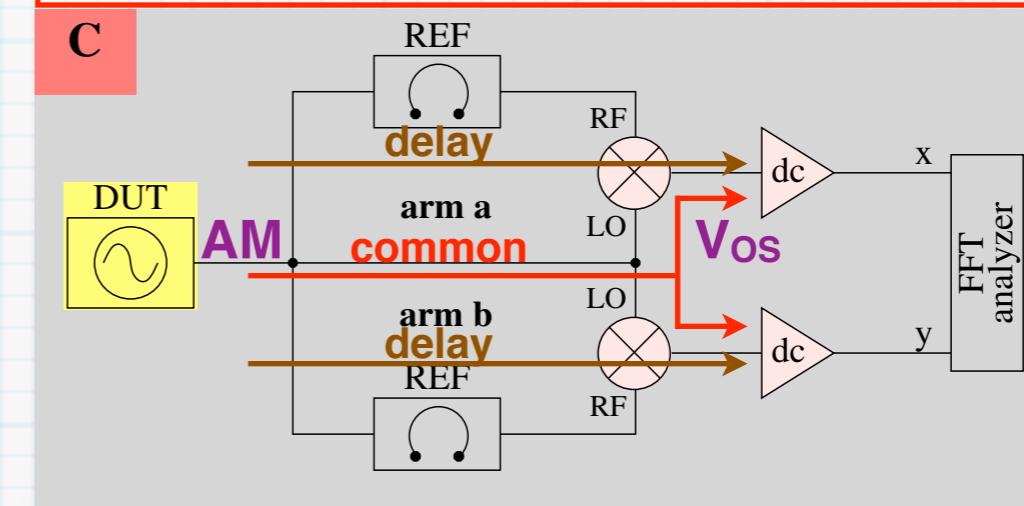The delay de-correlates the two inputs, so there is no sweet point



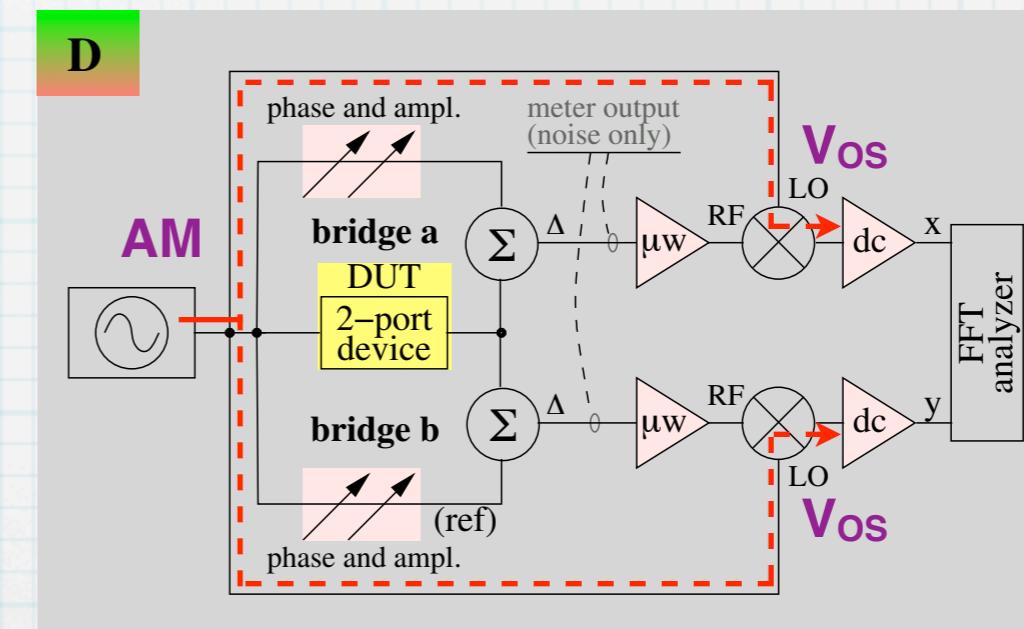
Should set both channels at the sweet point of the RF input, if exists, by offsetting the PLL or by biasing the IF



The effect of the AM noise is strongly reduced by the RF amplification

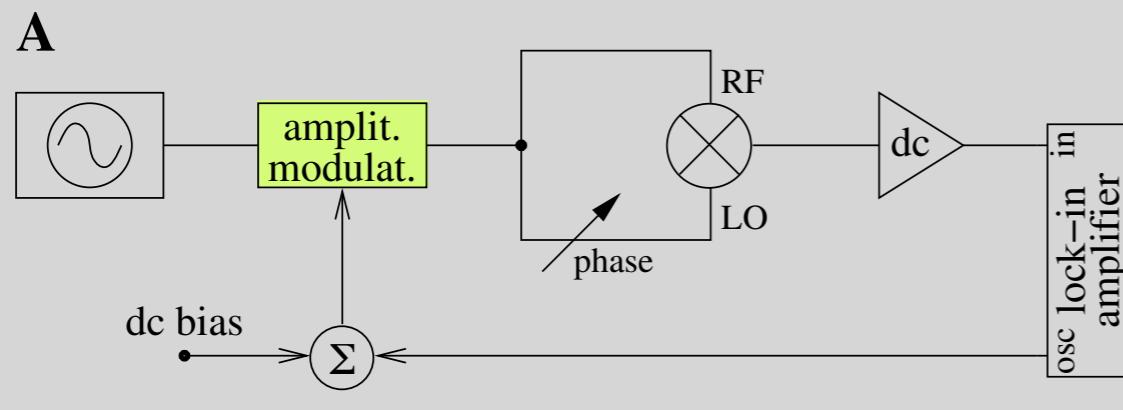
# Measurement of the mixer sensitivity to AM

- The measurement schemes follow immediately from the statement of the problem
- A lock-in amplifier is used for highest noise immunity
- Set the amplitude modulator to the **minimum of residual PM** (at least in the scheme B-C)




**LO & RF → IF:  
coefficient  $k_{lr}$**
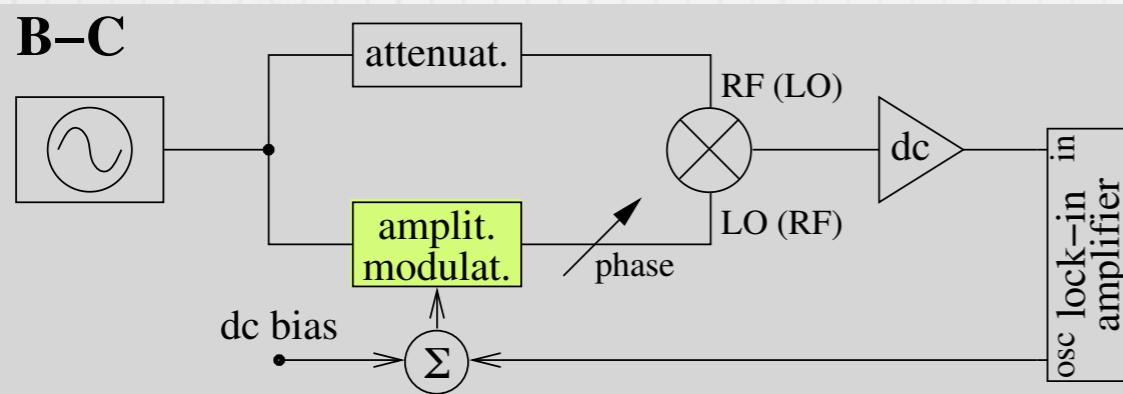
$$v_o(t) = k_\varphi \varphi(t) + k_{lr} \alpha(t)$$



**LO or RF → IF:  
coefficients  $k_l$  and  $k_r$**

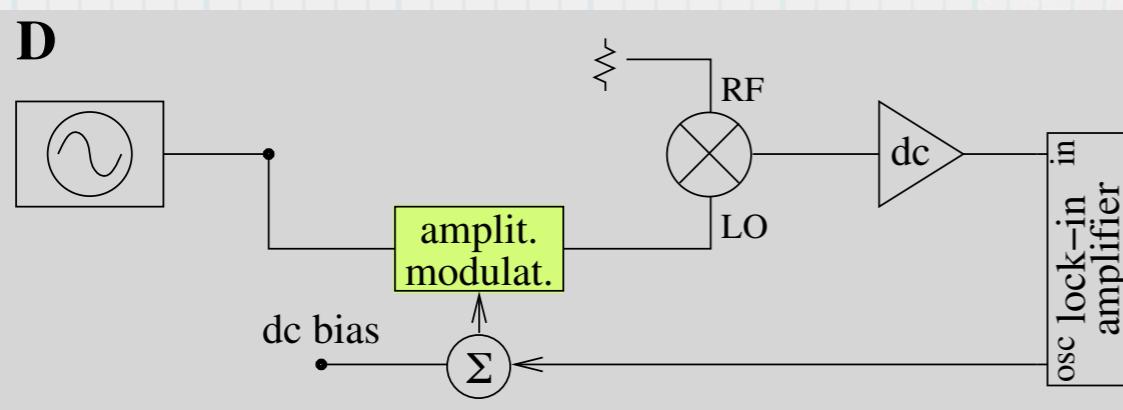
$$v_o(t) = k_\varphi \varphi(t) + k_l \alpha_l(t) + k_r \alpha_r(t)$$




**LO → IF in a sync.-detection  
scheme: coefficient  $k_{sd}$**

$$v_o(t) = k_\varphi \varphi(t) + k_{sd} \alpha(t)$$

# Example of results (microwave mixers)




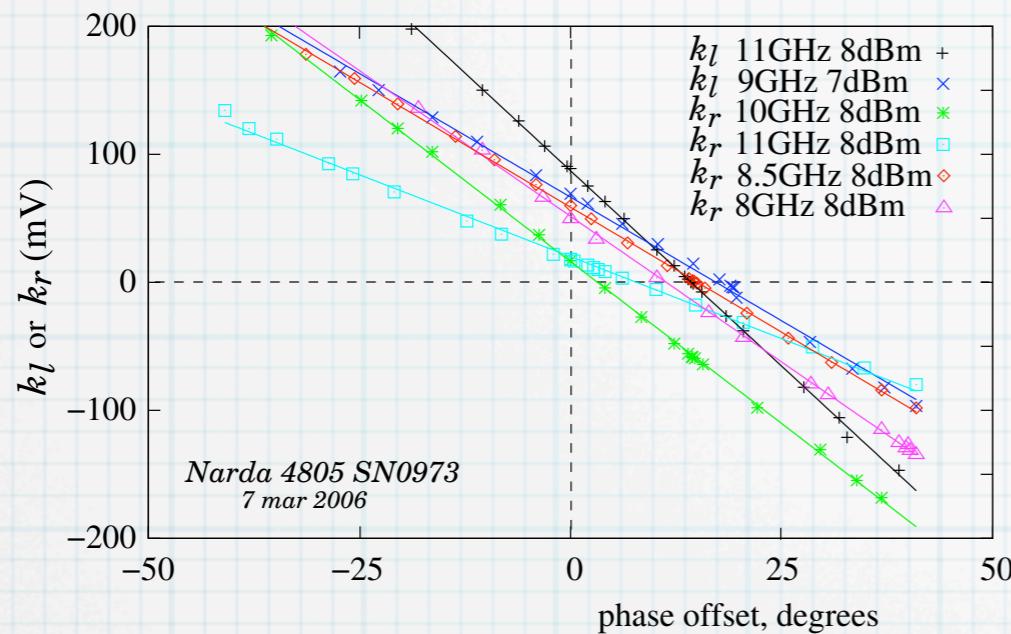


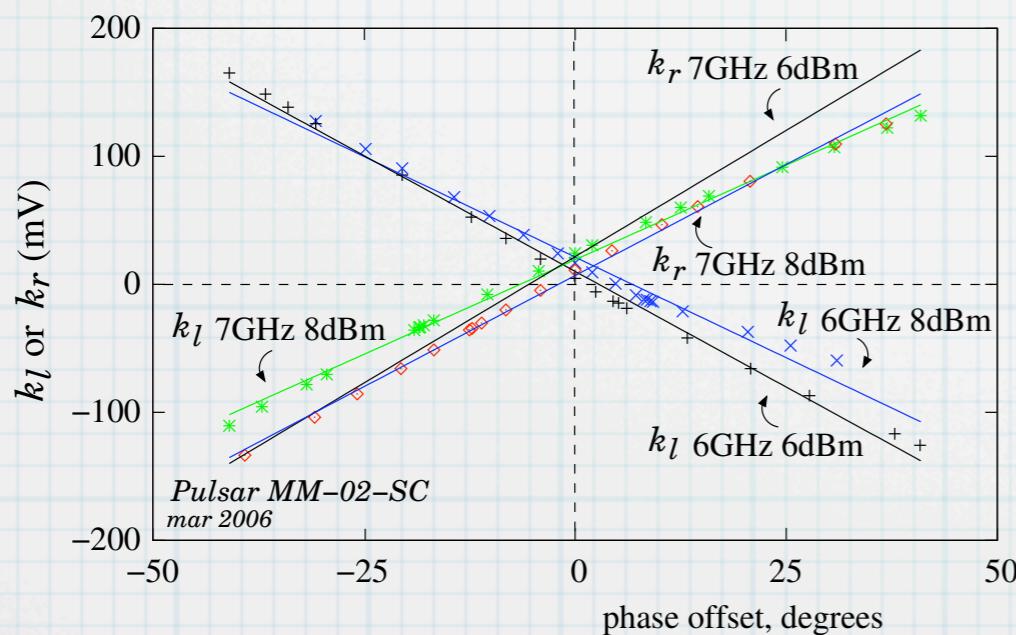The AM sensitivity depends on frequency.  
This is ascribed to the microstrip baluns,  
and to the diode capacitances



The AM sensitivity can have opposite sign  
at the two inputs

# Example of results (microwave mixers)

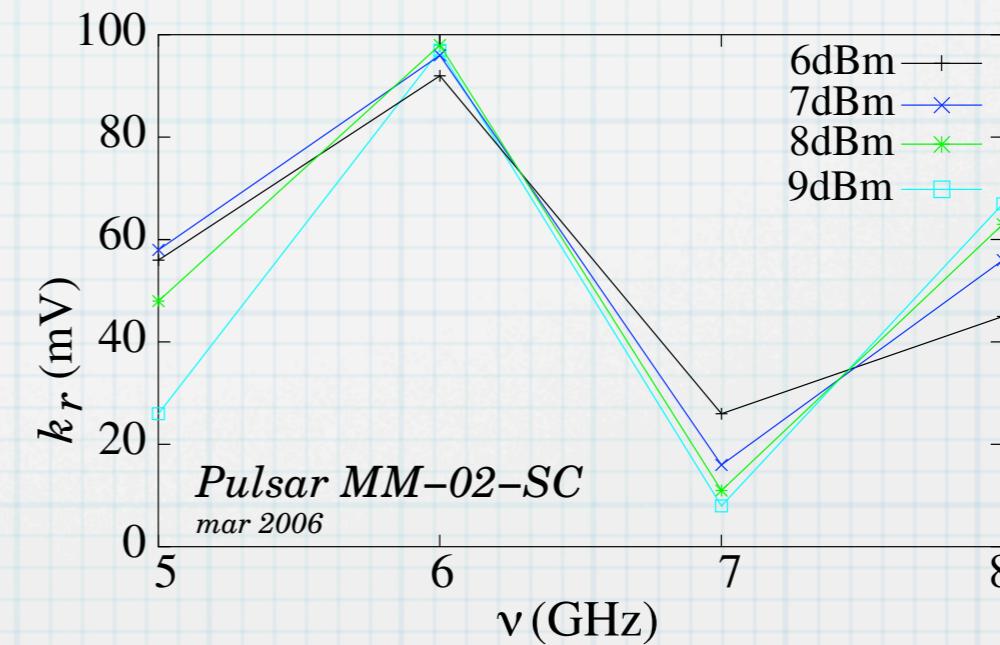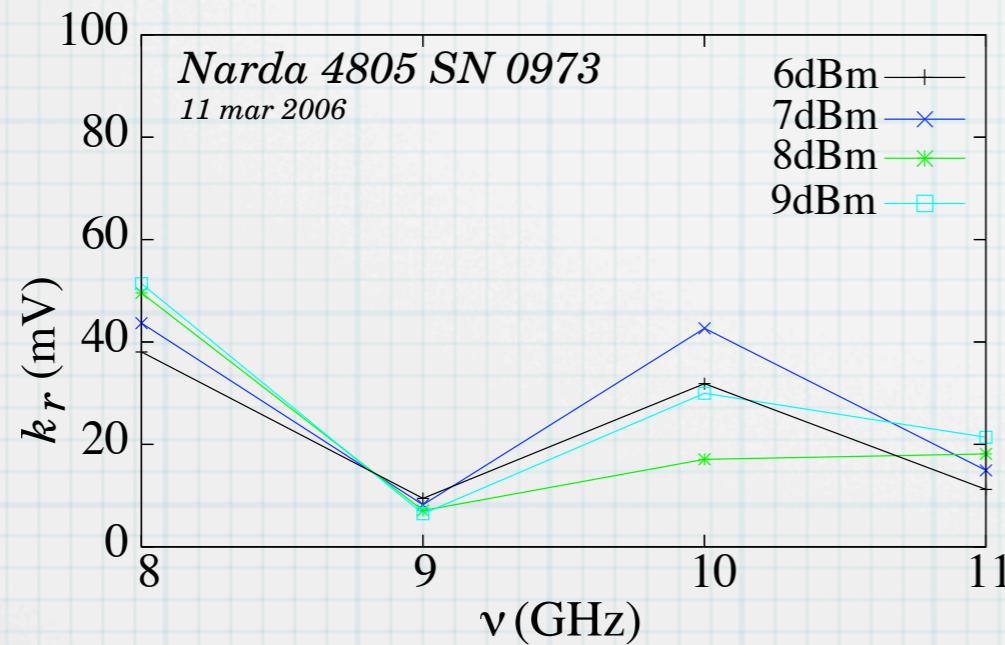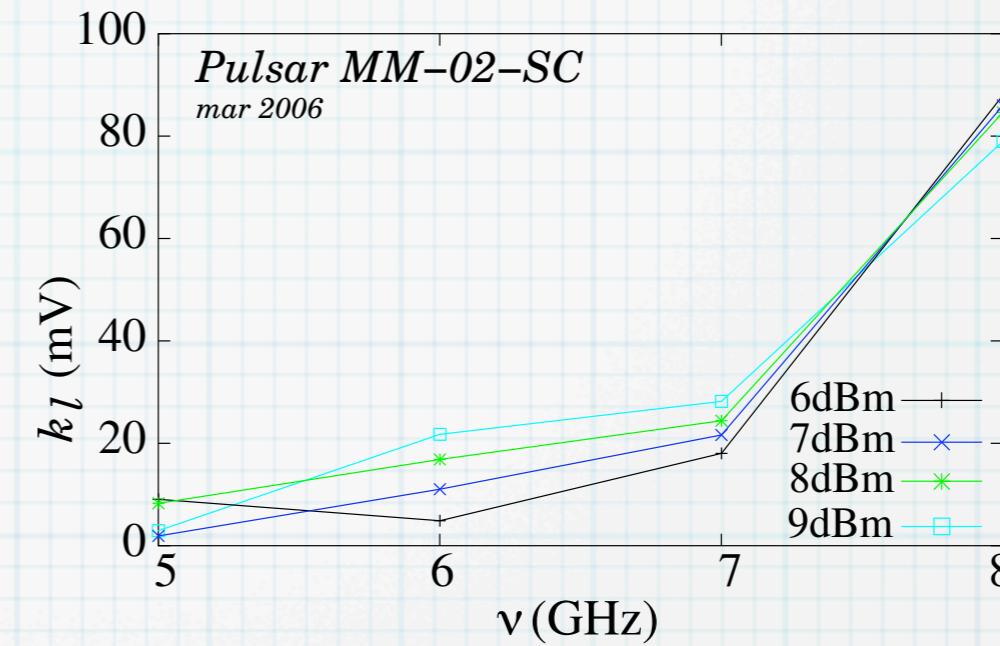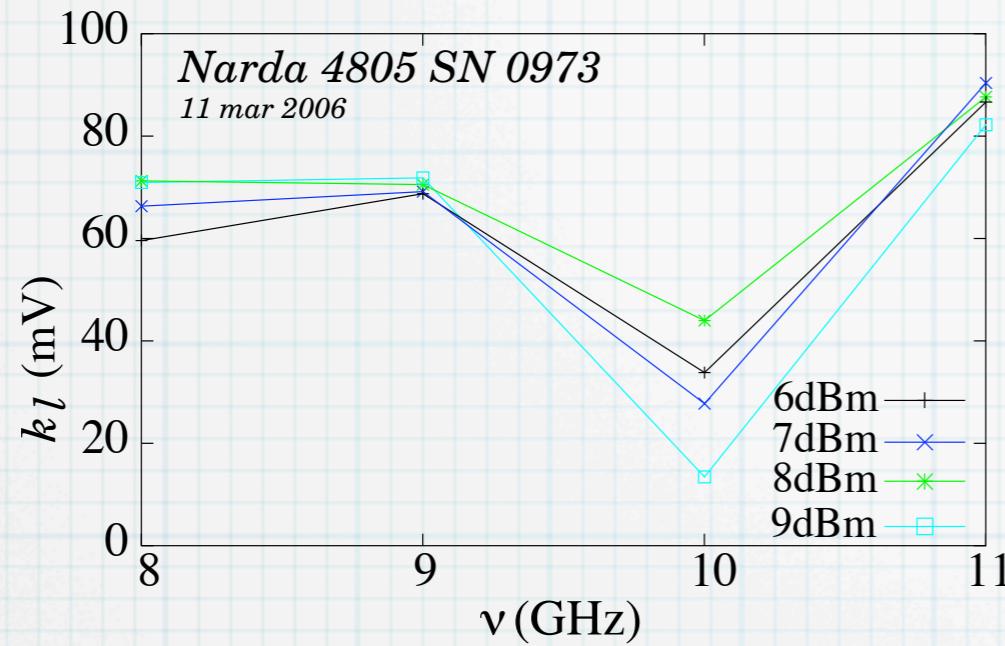

The effect of power is somewhat weaker than that of frequency

# Example of results (microwave mixers)





Mixer	$k_\varphi$	$k_{lr}$	$k_r$	$k_l$	$k_{sd}$
Narda 4805 s.no. 0972	272	16	7.9	37	6.5
Narda 4805 s.no. 0973	274	18.3	17.1	44	9.8
NEL 20814	279	51.5	12.1	37.9	2.7
NEL 20814	305	41	1.9	30.2	3.73
unit	mV/rad	mV	mV	mV	mV

Test parameters:  $\nu_0 = 10$  GHz,  $P = 6.3$  mW (8 dBm)

## Some relevant facts


- The AM noise rejection is of 15–40 dB
- Generally,  $k_{sd}$  is smaller than the other coefficients
- There is no predictable relation between  $k_\varphi$ ,  $k_l$ ,  $k_r$ ,  $k_{lr}$ , and  $k_{sd}$
- It is observed that  $k_{lr} \neq k_l + k_r$

# Example of results (VHF mixers)

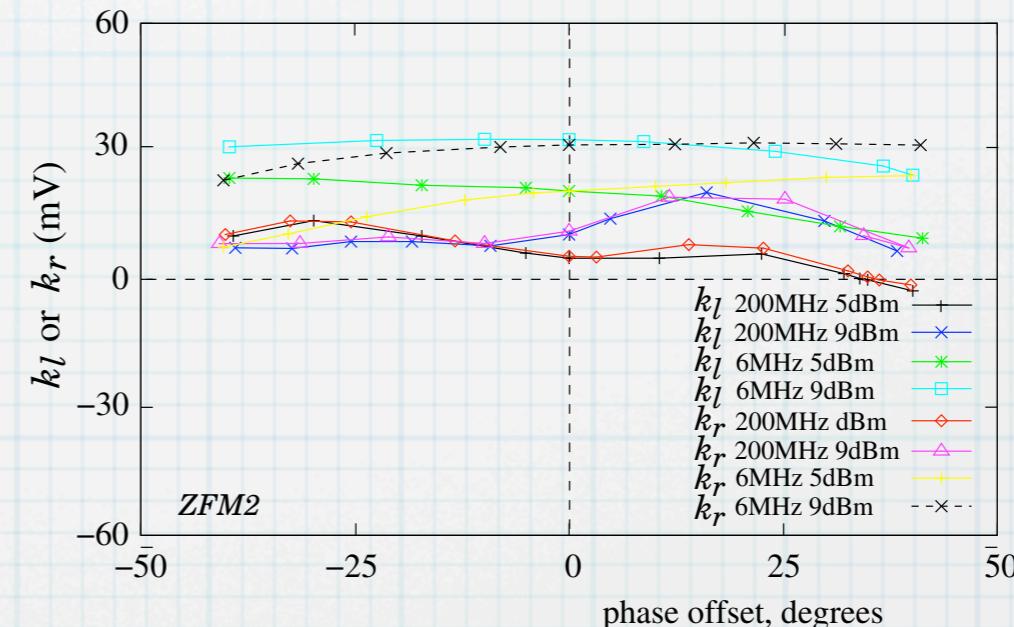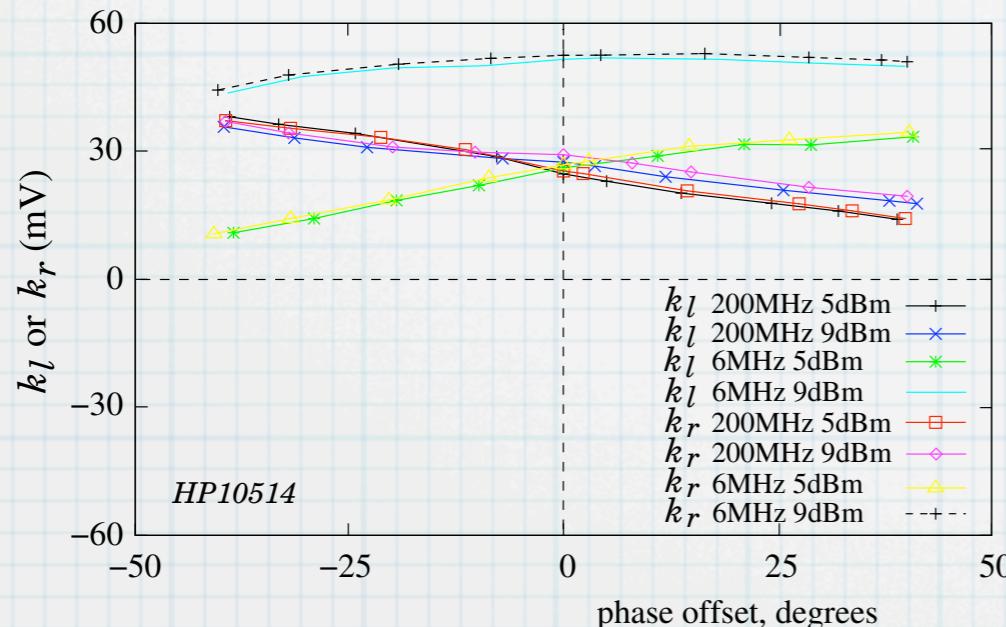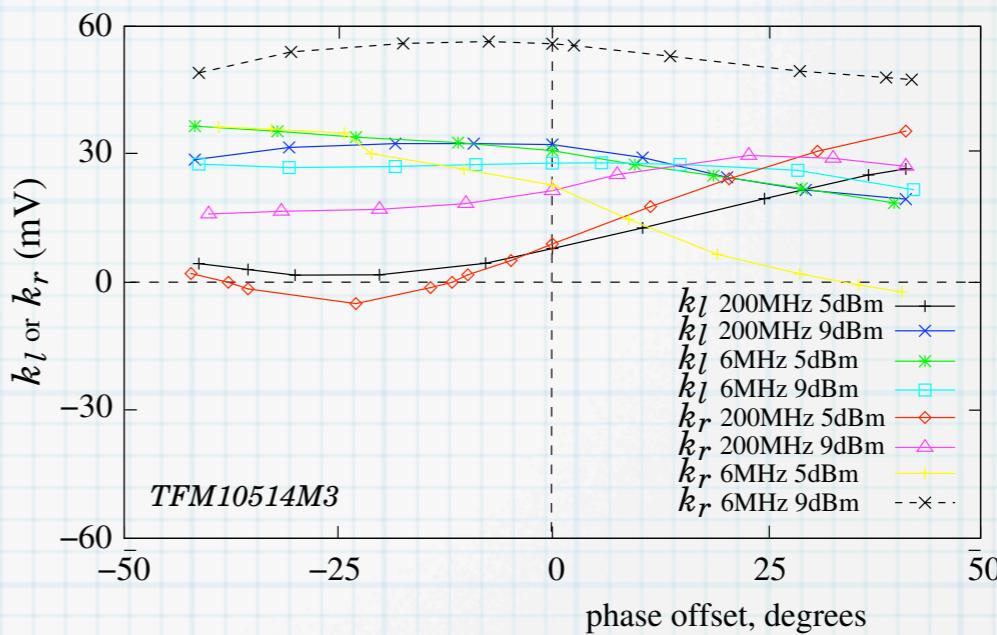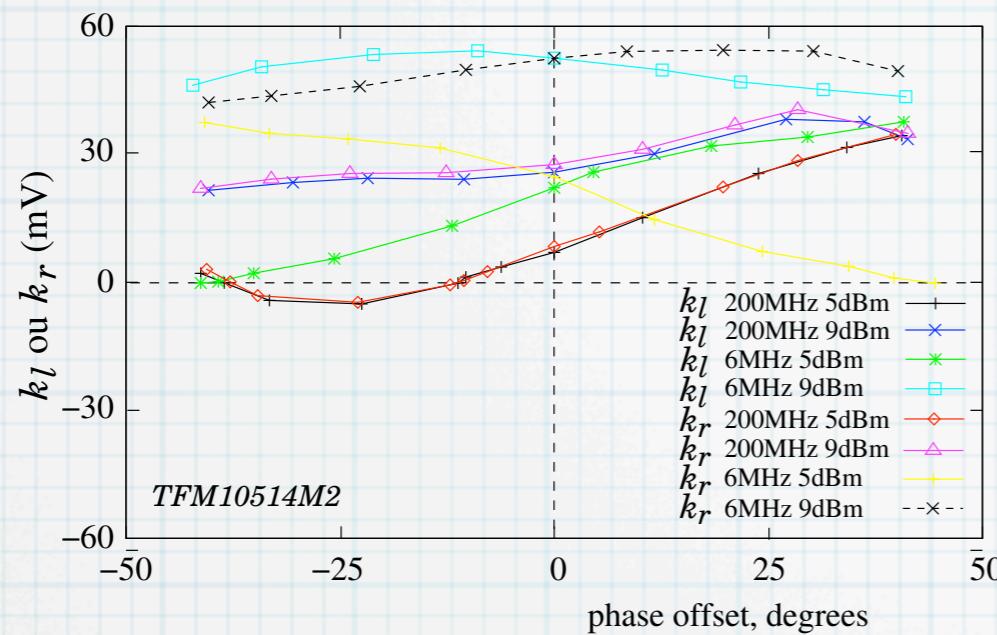

- The AM noise rejection is of 15–40 dB
- The sweet point is not observed in general
- There is no predictable relation between  $k_\varphi$ ,  $k_l$ ,  $k_r$ , ( $k_{lr}$ , and  $k_{sd}$  are not reported)
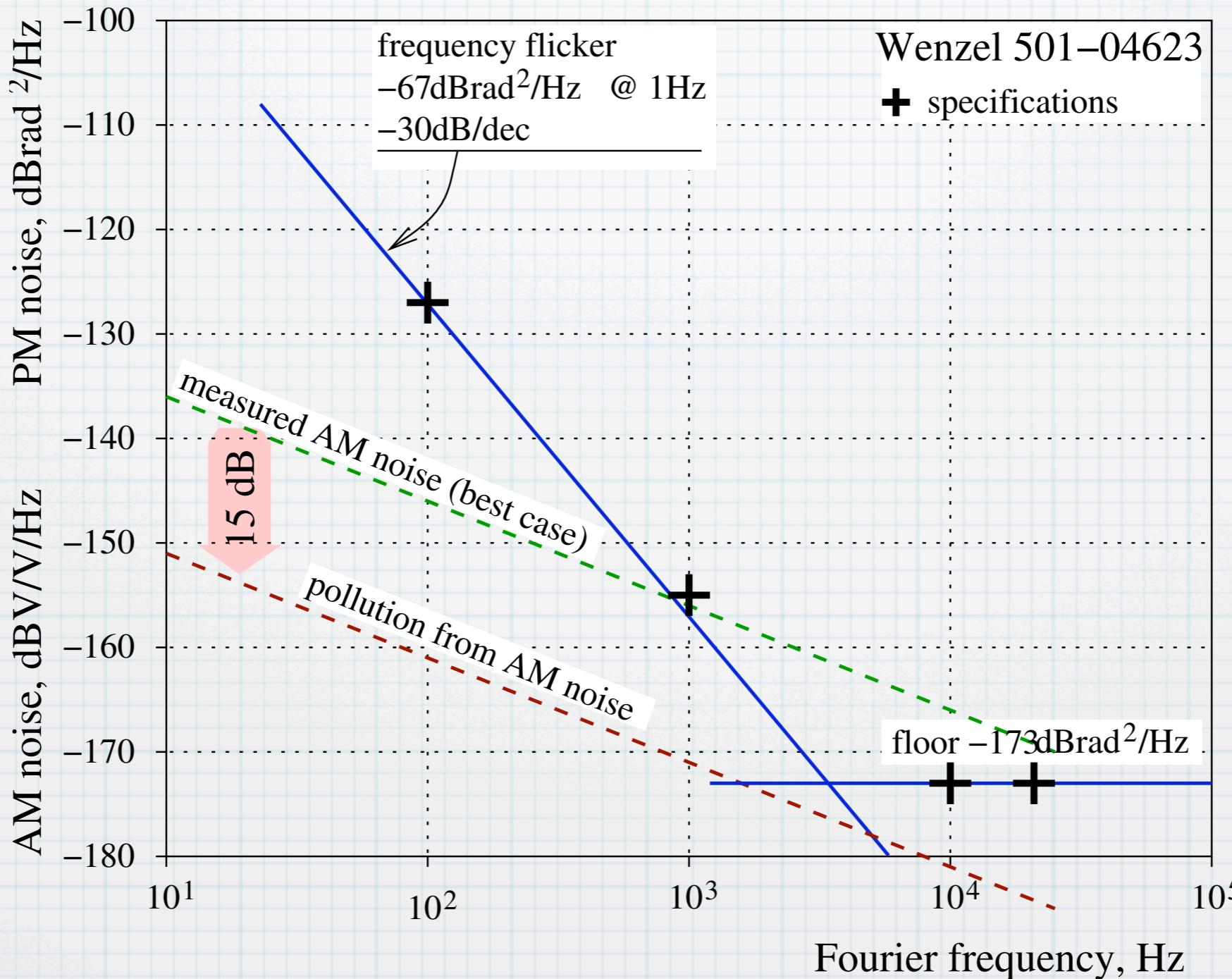
# Warning: even in single-channel measurements, the pollution from AM noise may be not that small




# Summary (1)

- \* The AM noise is taken in via the DC-offset sensitivity to the power
- \* The AM noise rejection is of 15-40 dB
- \* For a given mixer, there is no predictable relation between the AM noise sensitivity in different configurations
- \* The sweet point exists only in some configurations
- \* The sweet point is generally not observed in VHF mixers
- \* In correlation systems, rejecting the AM noise is possible only in some cases
- \* The AM noise can even limit the single-channel measurements

home page <http://rubiola.org>



Free downloads (texts and slides)
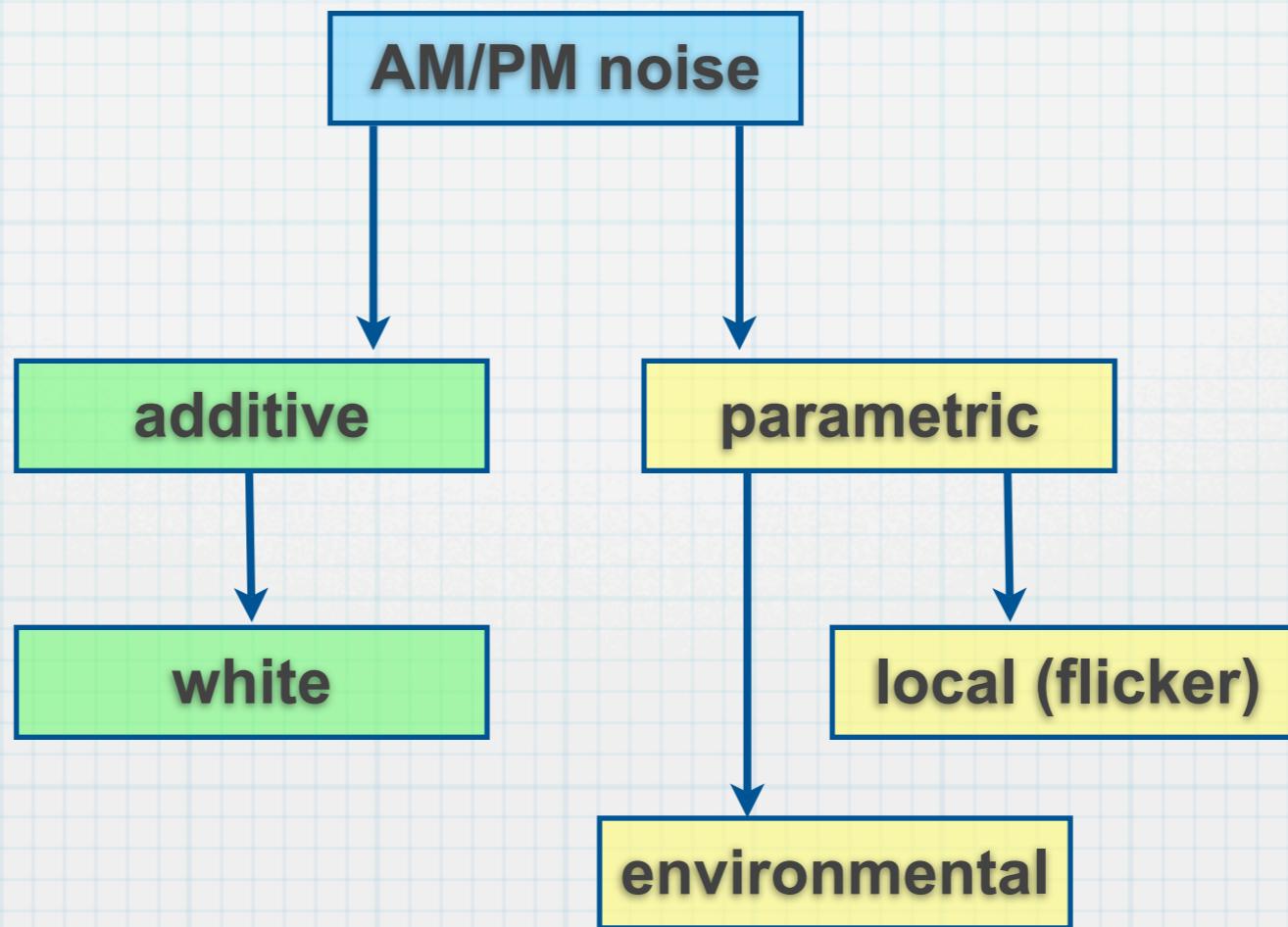
# 2 - On the $1/f$ noise in RF and microwave amplifiers



# Amplifier white noise

Noise figure F, Input power  $P_0$

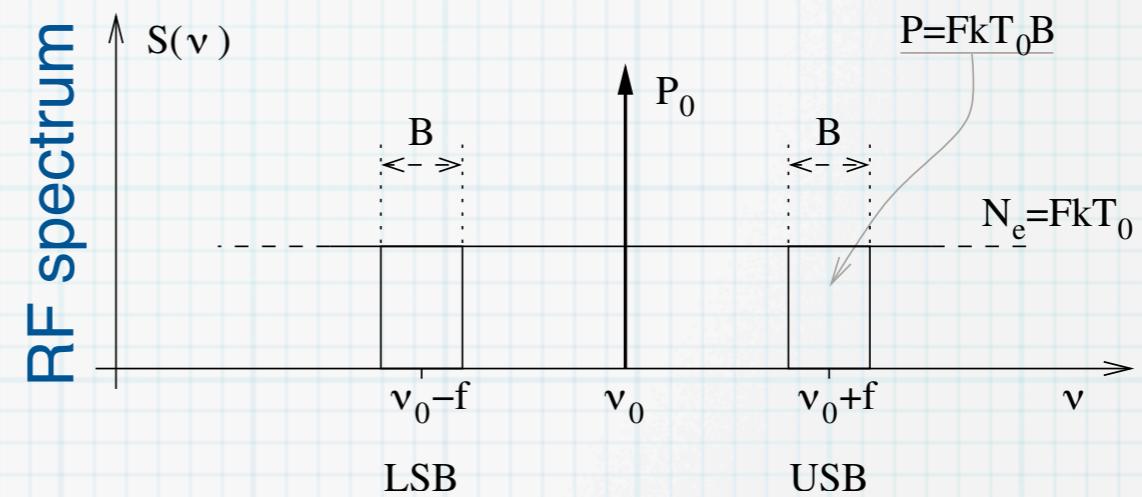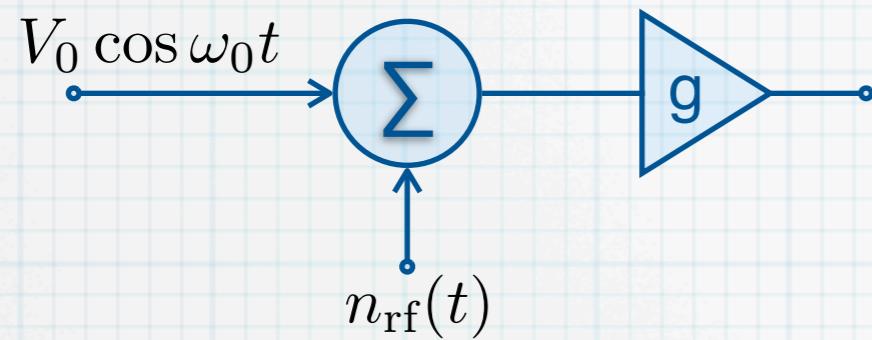


power law

$$S_\varphi = \sum_{i=-4}^0 b_i f^i$$


white  
phase noise

$$b_0 = \frac{F k T_0}{P_0}$$

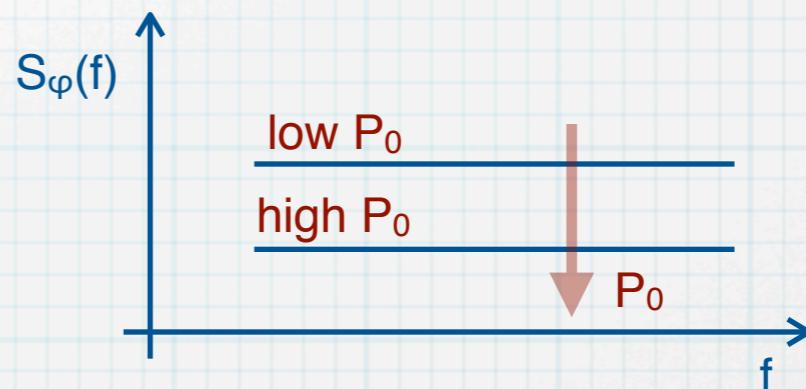
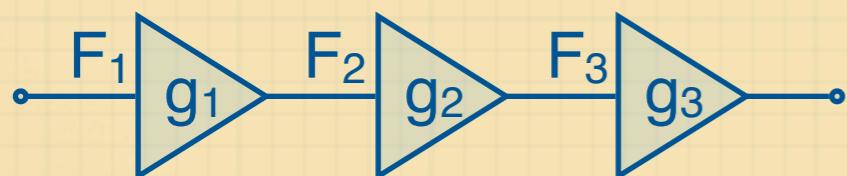
## Cascaded amplifiers (Friis formula)

The (phase) noise is chiefly that of the 1st stage




$$N = F_1 k T_0 + \frac{(F_2 - 1) k T_0}{g_1^2} + \dots$$

## The Friis formula applied to phase noise

$$b_0 = \frac{F_1 k T_0}{P_0} + \frac{(F_2 - 1) k T_0}{P_0 g_1^2} + \dots$$

# Amplifier flicker noise

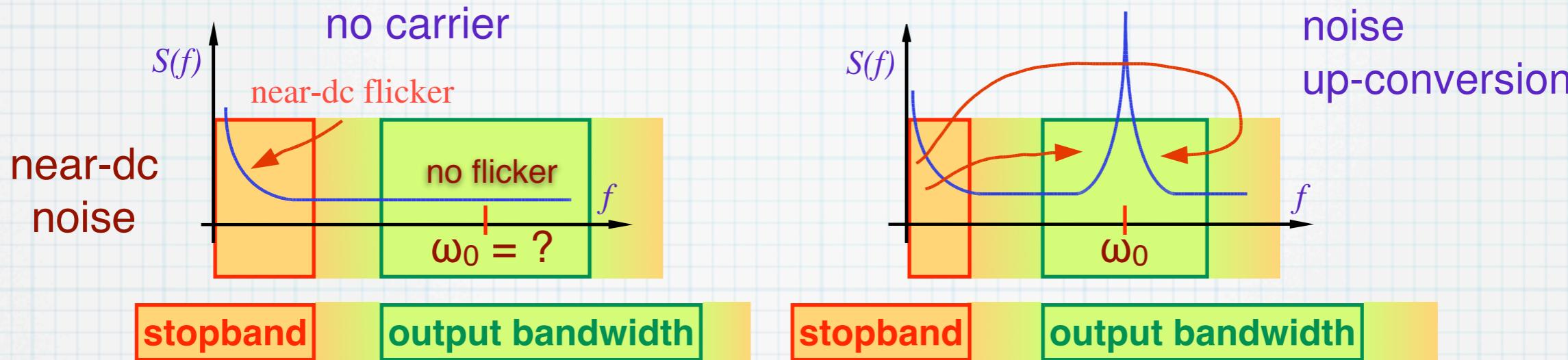

**carrier      near-dc noise**

$$v_i(t) = V_i e^{j\omega_0 t} + n'(t) + jn''(t)$$

**non-linear (parametric)amplifier**

**substitute**  
(careful, this hides the down-conversion)

$$v_o(t) = a_1 v_i(t) + a_2 v_i^2(t) + \dots$$

the parametric nature of I/f noise is hidden in  $n'$  and  $n''$

expand and select the  $\omega_0$  terms

$$v_o(t) = V_i \left\{ a_1 + 2a_2 [n'(t) + jn''(t)] \right\} e^{j\omega_0 t}$$


The noise sidebands are proportional to the input carrier

get AM and PM noise

$$\alpha(t) = 2 \frac{a_2}{a_1} n'(t) \quad \varphi(t) = 2 \frac{a_2}{a_1} n''(t)$$

The AM and the PM noise are independent of  $V_i$ , thus of power


# Amplifier flicker noise

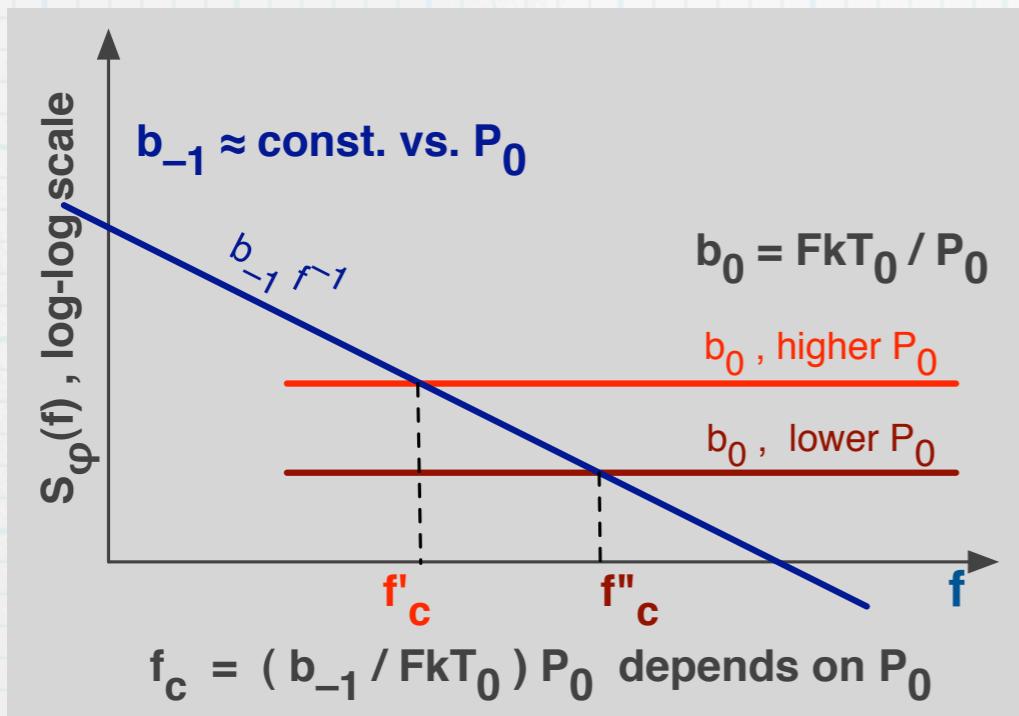


typical amplifier phase noise			
RATE	GaSs HBT microwave	SiGe HBT microwave	Si bipolar HF/UHF
fair	-100		-120
good	-110	-120	-130
best	-120	-130	-150
	unit dBrad <sup>2</sup> /Hz		

- \* The phase flicker coefficient  $b_{-1}$  is about independent of power.
- \* Hence, describing the  $1/f$  noise in terms of  $f_c$  is misleading because  $f_c$  depends on the input power



# Amplifier flicker noise – experiments

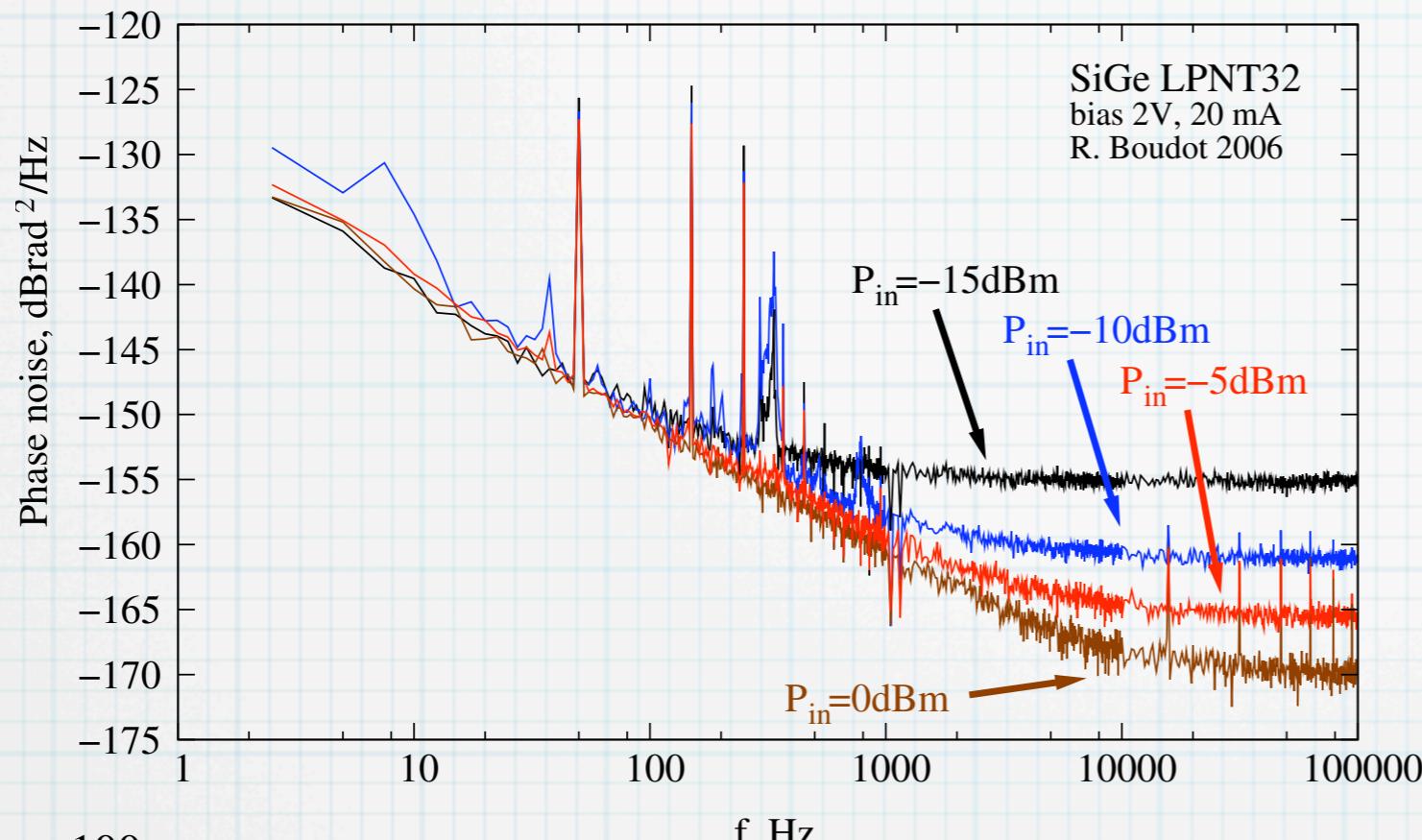

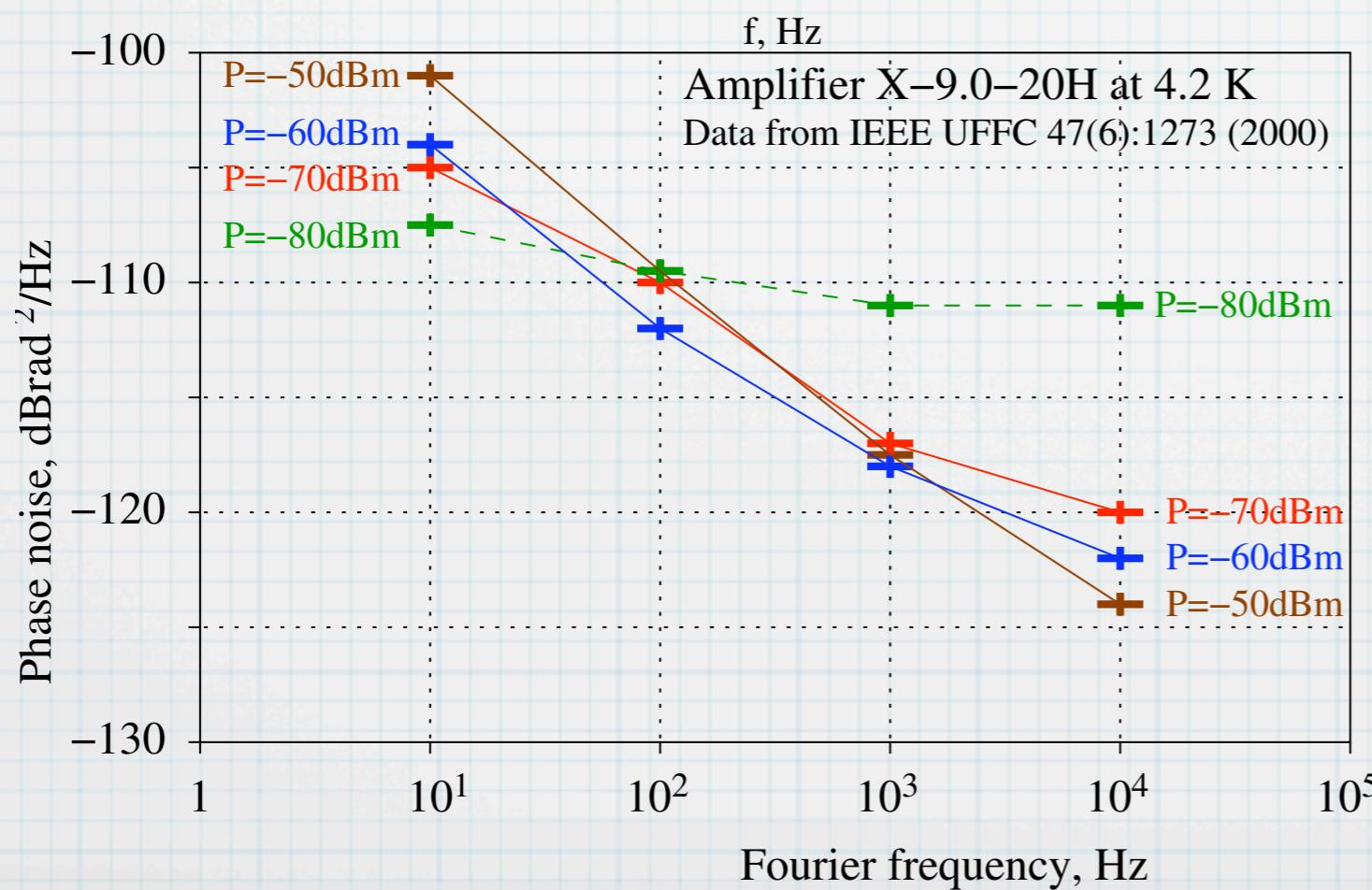- \* The  $1/f$  phase noise  $b_{-1}$  is about independent of power
- \* The white noise  $b_0$  scales up/down as  $1/P_0$ , i.e., the inverse of the carrier power



# Flicker noise in cascaded amplifiers

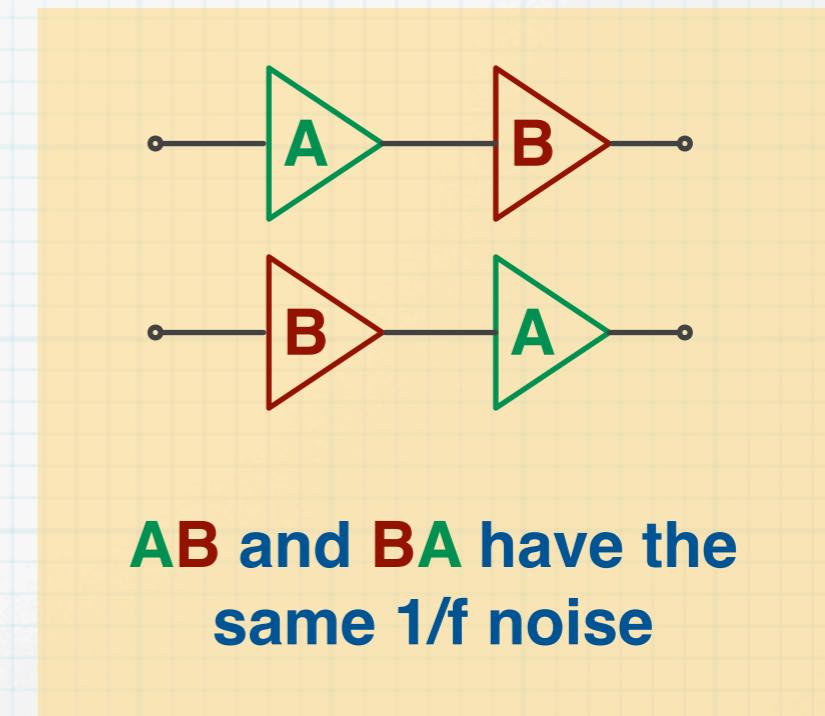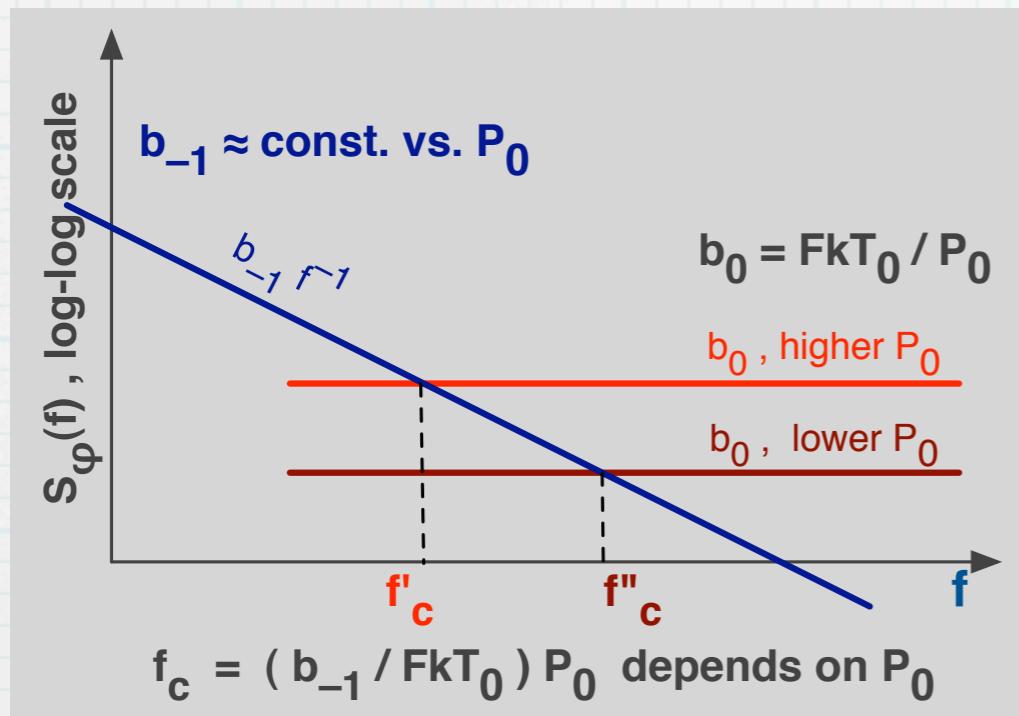

The phase flicker coefficient  $b_{-1}$  is about independent of power. Hence:


- \* in a cascade,  $(b_{-1})_{\text{tot}}$  does not depend of the amplifier order
- \* in practice, in a cascade each stage contributes about equally

$$(b_{-1})_{\text{tot}} = \sum_{i=1}^m (b_{-1})_i$$


m cascaded amplifiers

- \*  $b_{-1}$  is roughly proportional to the gain through the number of stages

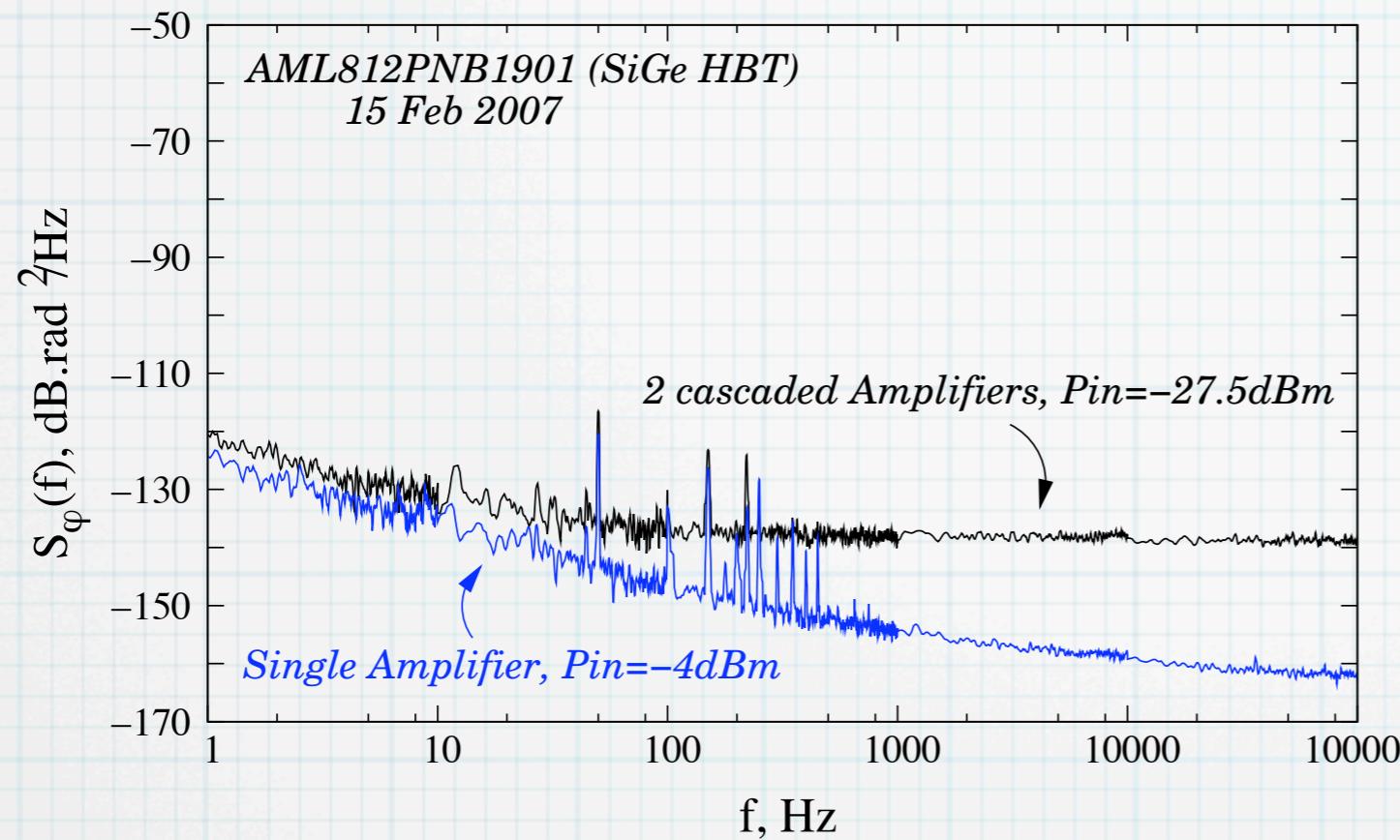
# Flicker in cascaded amplifiers – experiments



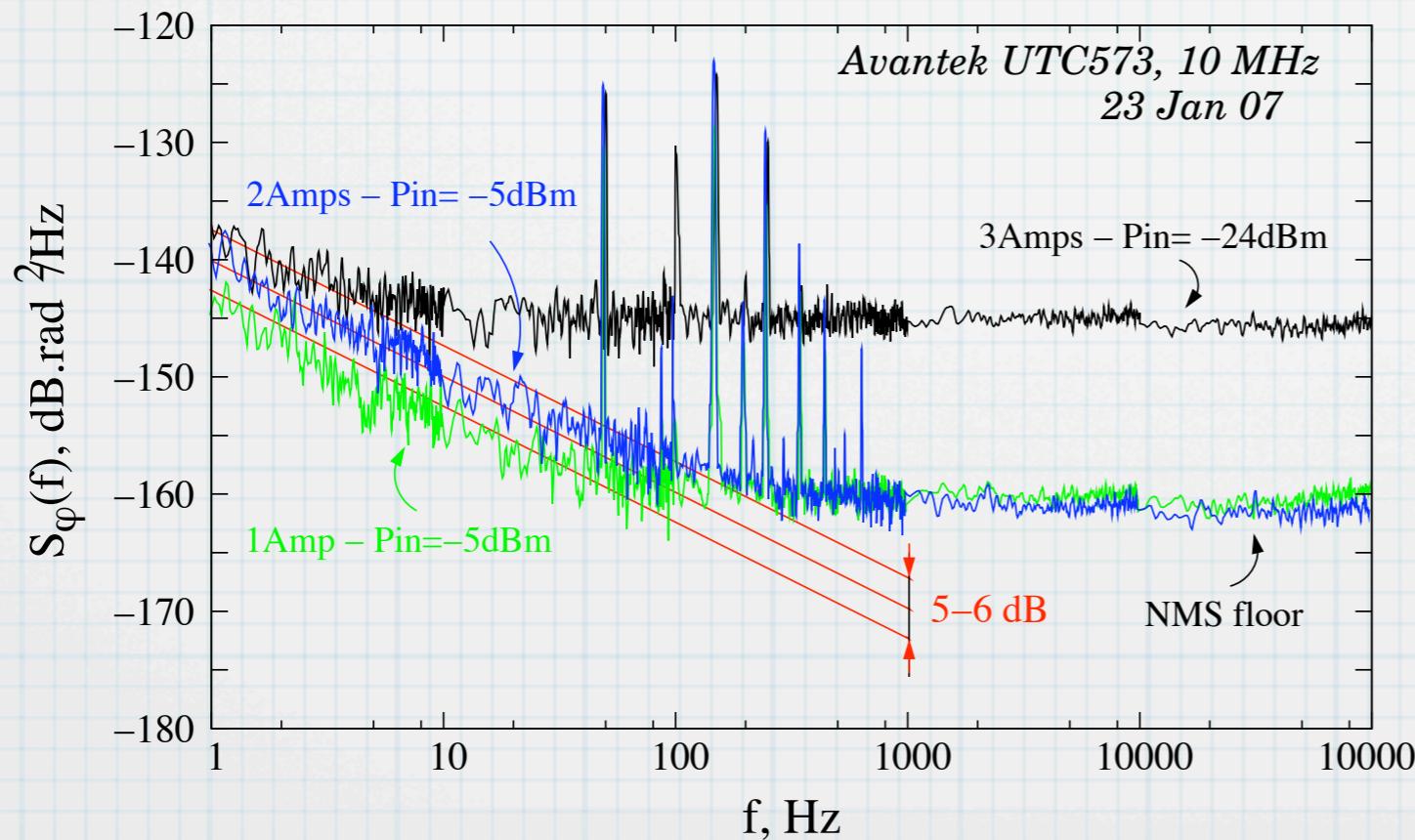The expected flicker of a cascade increases by:  
**3 dB, with 2 amplifiers**  
**5 dB, with 3 amplifiers**



# Flicker noise in parallel amplifiers

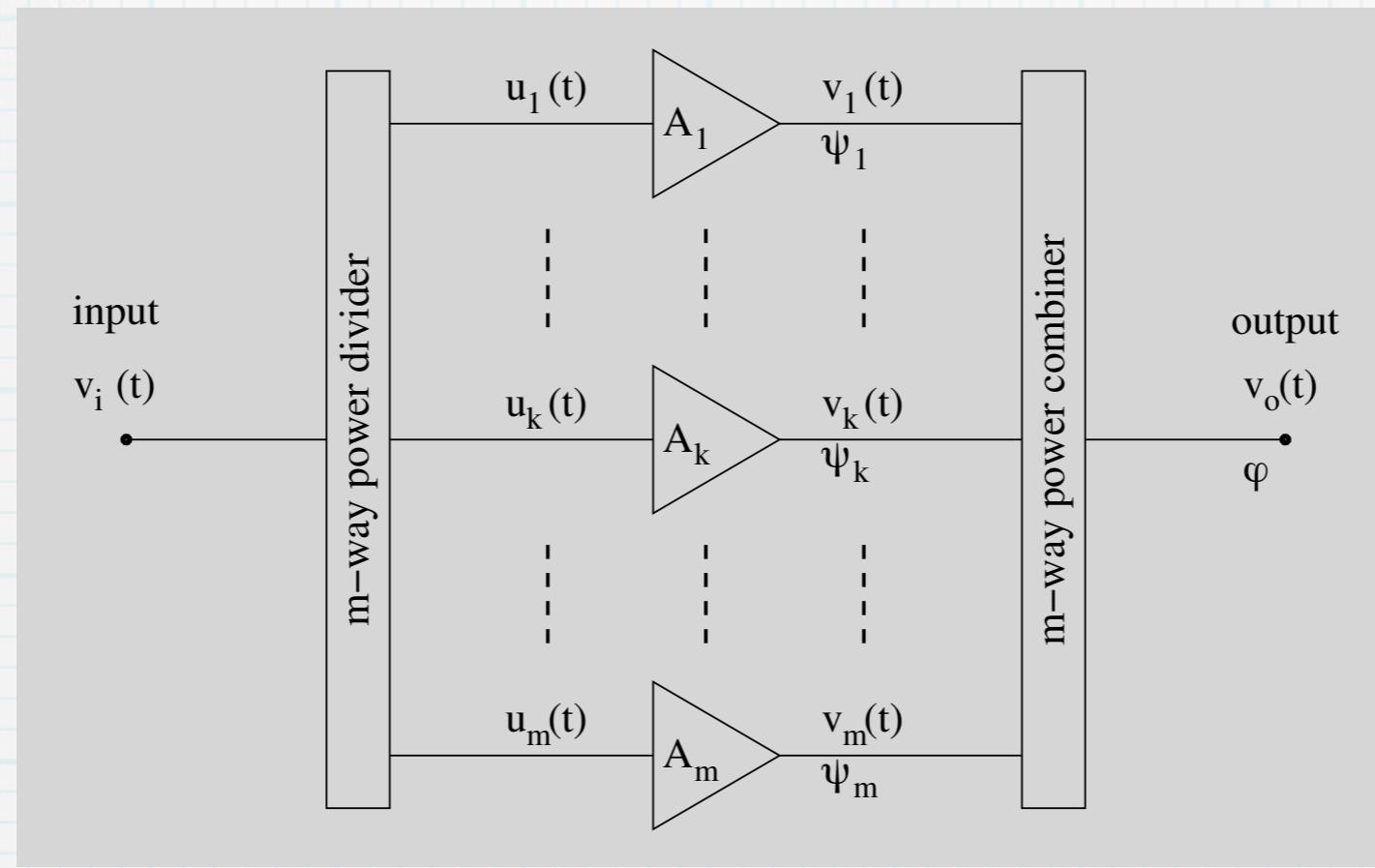

- \* The phase flicker coefficient  $b_{-1}$  is about independent of power
- \* The flicker of a branch is not increased by splitting the input power
- \* At the output,
  - \* the carrier adds up coherently
  - \* the phase noise adds up statistically
- \* Hence, the  $1/f$  phase noise is reduced by a factor  $m$
- \* Only the flicker noise can be reduced in this way

$$b_{-1} = \frac{1}{m} [b_{-1}]_{\text{branch}}$$

**Gedankenexperiment:** join the  $m$  branches of a parallel amplifier forming a single large active device: the phase flickering is proportional to the inverse physical size of the amplifier active region

# Parallel amplifiers, mathematics

$$u_k(t) = \frac{1}{\sqrt{m}} v_i(t)$$

$$v_o(t) = \frac{1}{\sqrt{m}} \sum_{k=1}^m v_k(t)$$

$$v_k(t) = \frac{1}{\sqrt{m}} V_i \left\{ a_1 + 2a_2 [n'_k(t) + j n''_k(t)] \right\} e^{j2\pi\nu_0 t}$$

$$\psi_k(t) = 2 \frac{a_2}{a_1} n''_k(t)$$

$$\varphi_k(t) = \frac{\frac{1}{m} V_i 2a_2 n''_k(t) e^{j2\pi\nu_0 t}}{a_1 V_i e^{j2\pi\nu_0 t}}$$

$$= \frac{1}{m} 2 \frac{a_2}{a_1} n''_k(t)$$

$$S_\varphi(f) = \sum_{k=1}^m \frac{1}{m^2} 4 \frac{a_2^2}{a_1^2} S_{n''_k}(f)$$

$$S_\varphi(f) = \frac{1}{m} 4 \frac{a_2^2}{a_1^2} S_{n''}(f)$$

$$S_\varphi(f) = \frac{1}{m} S_\psi(f)$$


$$b_{-1} = \frac{1}{m} [b_{-1}]_{\text{branch}}$$

branch-amplifier input

input

$v_i(t)$

•

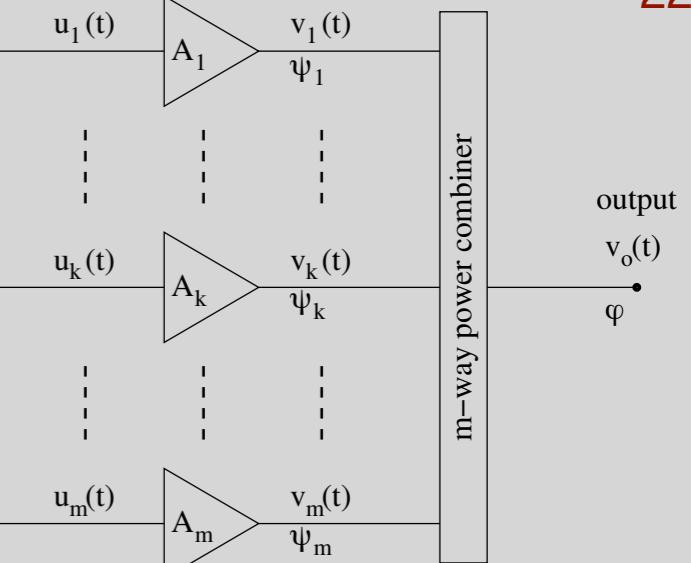

main output

branch → output


branch

branch → output


Σ branches → output

$m$  equal branches → output


# Flicker noise in parallel amplifiers

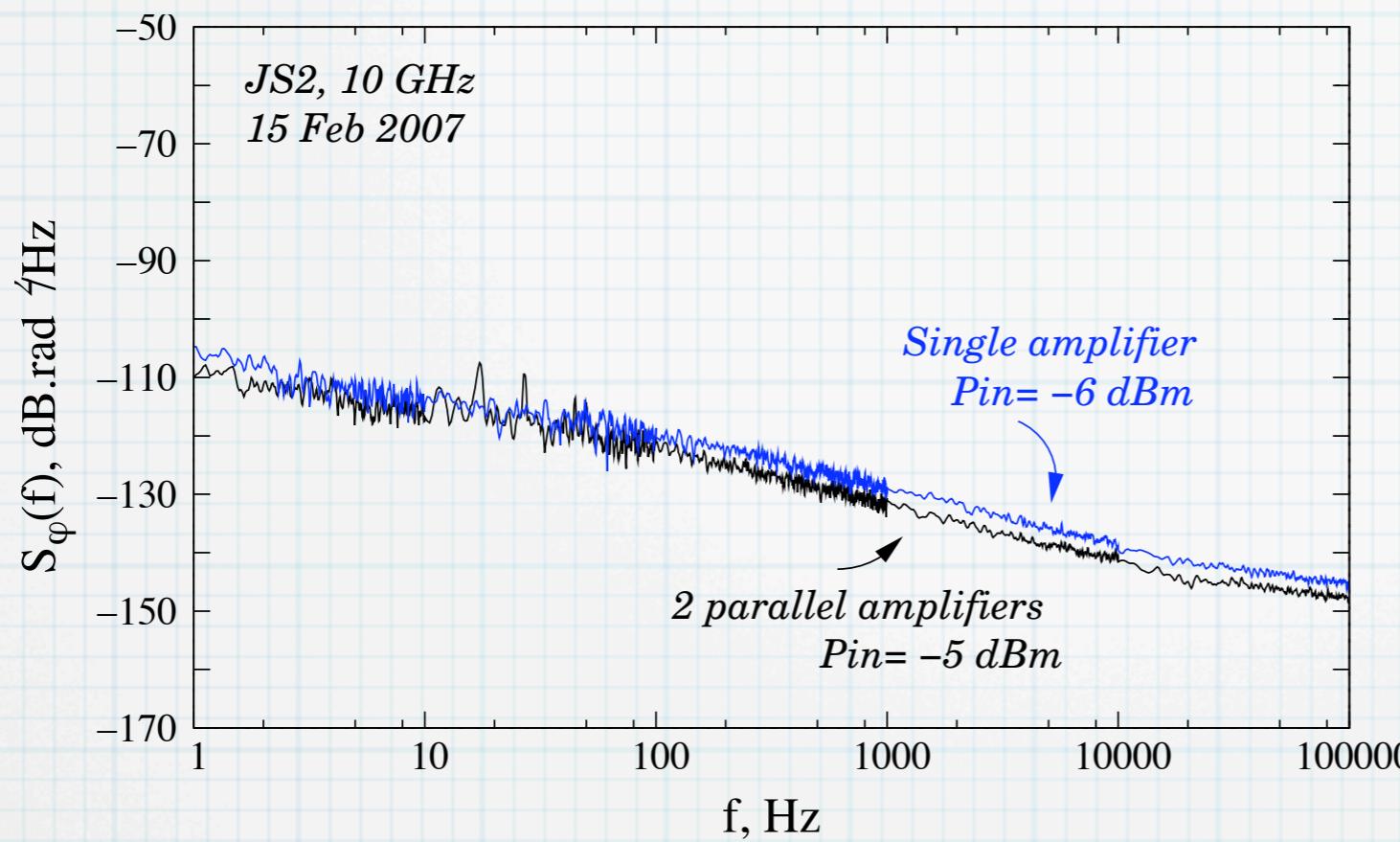

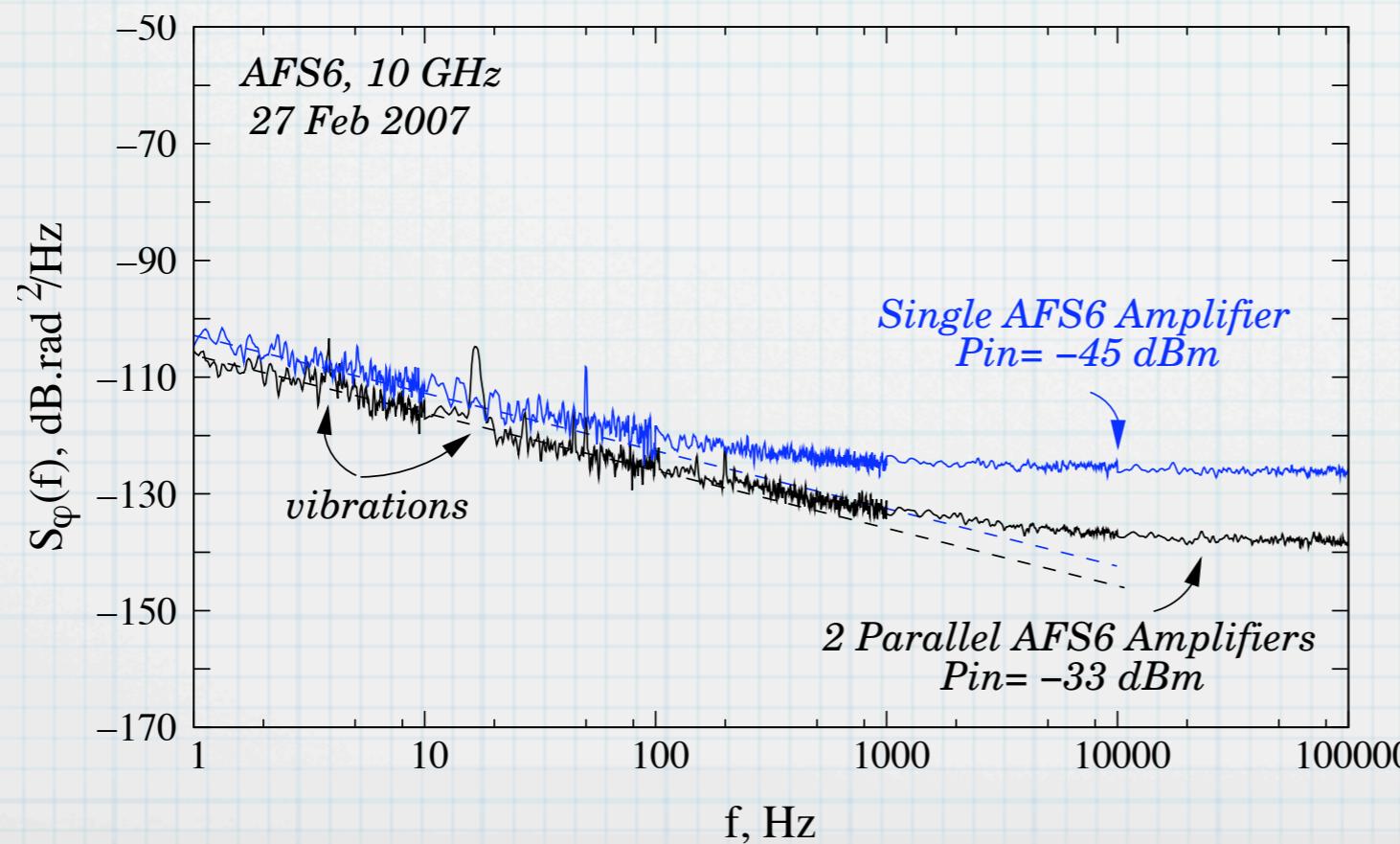**Connecting two amplifiers in parallel, the expected flicker is reduced by 3 dB**





# Flicker noise in parallel amplifiers

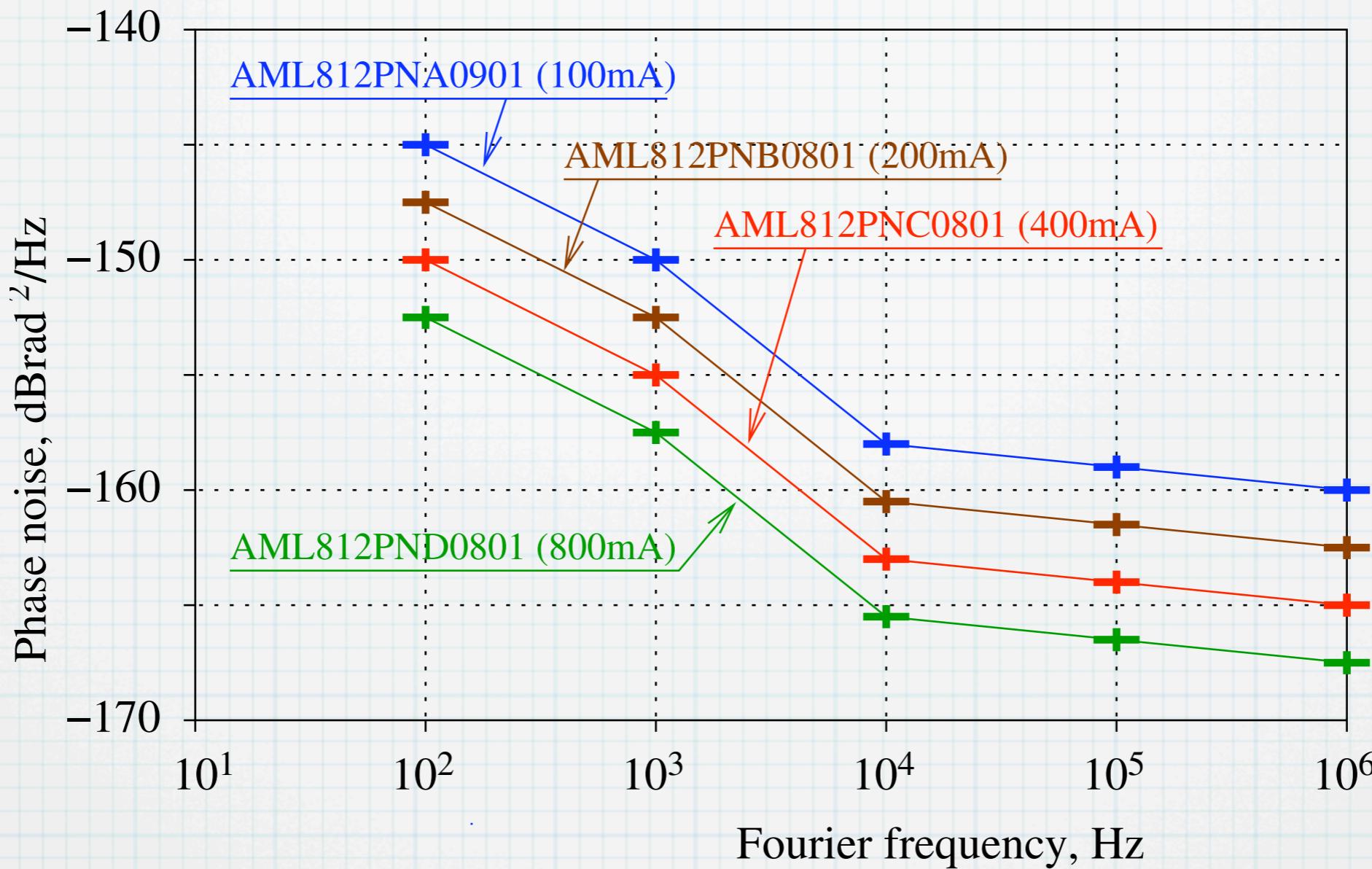

Specification of low phase-noise amplifiers (AML web page)								
amplifier	parameters				phase noise vs. $f$ , Hz			
	gain	$F$	bias	power	$10^2$	$10^3$	$10^4$	
AML812PNA0901	10	6.0	100	9	-145.0	-150.0	-158.0	-159.0
AML812PNB0801	9	6.5	200	11	-147.5	-152.5	-160.5	-161.5
AML812PNC0801	8	6.5	400	13	-150.0	-155.0	-163.0	-164.0
AML812PND0801	8	6.5	800	15	-152.5	-157.5	-165.5	-166.5
unit	dB	dB	mA	dBm	dB $\text{Brad}^2/\text{Hz}$			
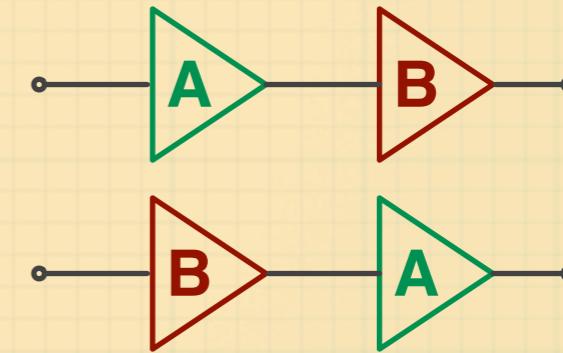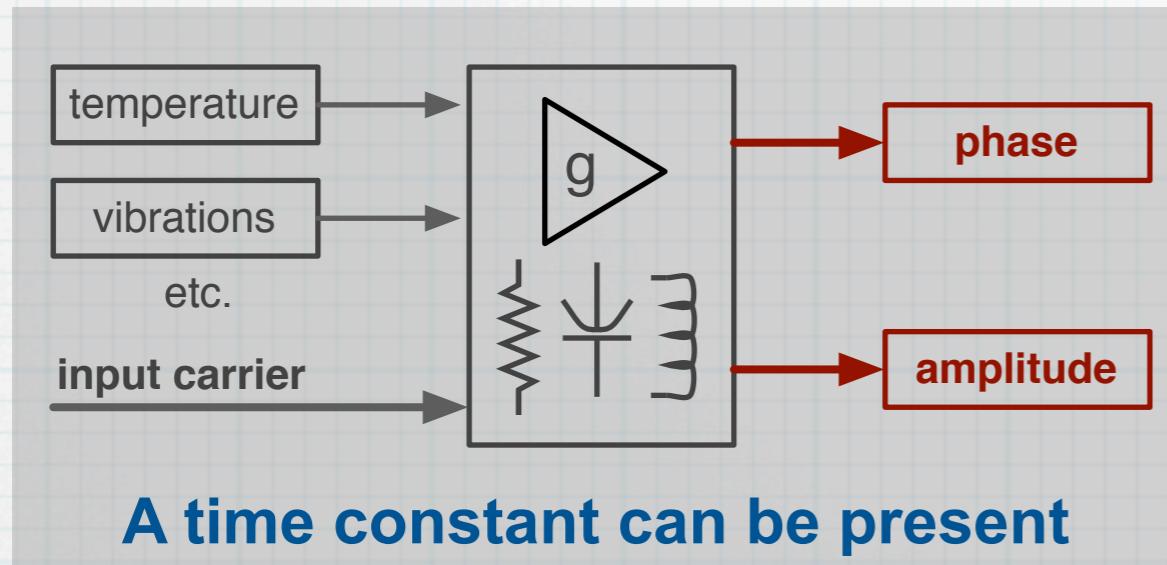
# Environmental (parametric) noise in amplifiers



$\varphi = \varphi_A + \varphi_B$  and  $\alpha = \alpha_A + \alpha_B$   
regardless of the amplifier order

Cascading  $m$  equal amplifiers,  $S_\alpha(f)$  and  $S_\varphi(f)$  increase by a factor  $m^2$ .

If the amplifier were independent,  $S_\alpha(f)$  and  $S_\varphi(f)$  would increase only by a factor  $m$ .


## Cascaded amplifiers

$$\text{let } z(t) = x(t) + y(t)$$

## Phase noise

$$\begin{aligned} S_z(f) &= ZZ^* \\ &= (X + Y)(X + Y)^* \\ &= XX^* + YY^* + XY^* + YX^* \\ &= S_x + S_y + \underbrace{S_{xy}}_{>0} + \underbrace{S_{yx}}_{>0} \end{aligned}$$

# Environmental effects in RF amplifiers

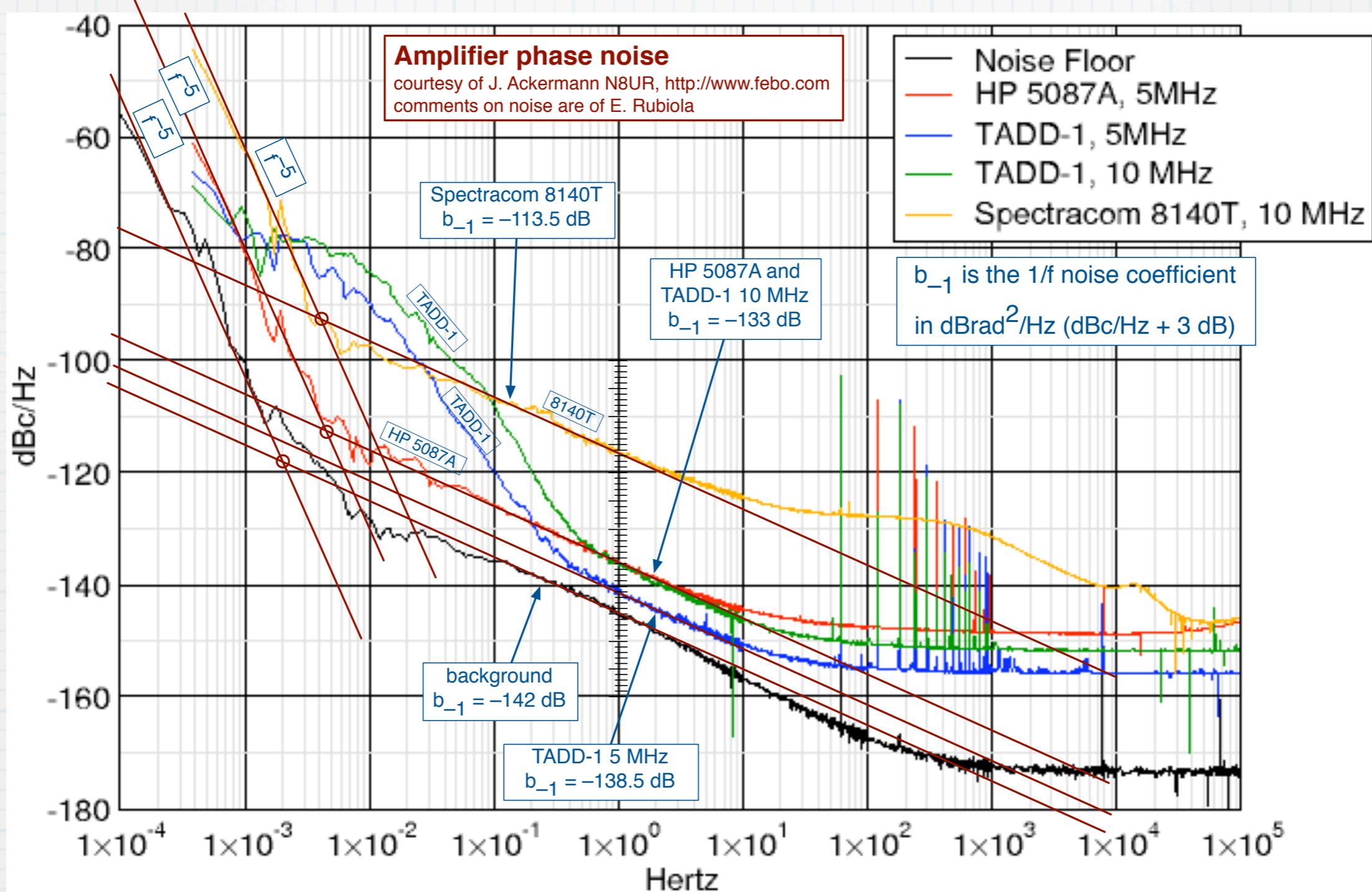

It is experimentally observed that the temperature fluctuations cause a spectrum  $S_\alpha(f)$  or  $S_\varphi(f)$  of the  $1/f^5$  type

Yet, at lower frequencies the spectrum folds back to  $1/f$

# Summary (2)

- \* Flicker AM/PM noise results from parametric modulation from the near-dc  $1/f$  noise
- \* The  $1/f$  noise coefficient  $b_{-1}$  is about independent of the carrier power
- \* Describing the  $1/f$  noise in terms of  $f_c$  is misleading
- \* Cascading  $m$  amplifiers, the  $1/f$  noise increases by a factor  $m$
- \* Connecting  $m$  amplifiers in parallel, the  $1/f$  noise drops by a factor  $m$
- \* Thermal fluctuations induce  $1/f^5$  PM noise, which folds back to  $1/f$  at lower frequencies

home page <http://rubiola.org>

Free downloads (texts and slides)